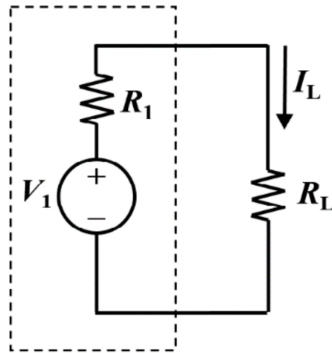


# CG1111A Tutorial 1

Prannaya Gupta

18<sup>th</sup> August 2022

1. Consider the following battery with open-circuit voltage  $V_1 = 12$  V, and internal resistance  $R_1 = 0.15$   $\Omega$ . Find the load current  $I_L$  and the corresponding power efficiency  $\eta_L$  for the following load:



- (a)  $R_L = 10$   $\Omega$

**Solution:**


$$\begin{aligned} I_L &= \frac{\varepsilon}{R_T} \\ &= \frac{V_1}{R_1 + R_L} \\ &= \frac{12}{0.15 + 10} \\ &= 1.18227 \\ &\approx \mathbf{1.18 \text{ A}} \\ \eta_L &= \frac{P_L}{P_S} \\ &= \frac{1.18227^2 \times 10}{1.18227 \times 12} \times 100\% \\ &= 98.712\% \\ &\approx \mathbf{98.7\%} \end{aligned}$$

- (b)  $R_L = 1$   $\Omega$

**Solution:**

$$\begin{aligned}
 I_L &= \frac{\varepsilon}{R_T} \\
 &= \frac{V_1}{R_1 + R_L} \\
 &= \frac{12}{0.15 + 1} \\
 &= 10.43478 \\
 &\approx \mathbf{1.18 \text{ A}} \\
 \eta_L &= \frac{P_L}{P_S} \\
 &= \frac{10.43478^2 \times 1}{10.43478 \times 12} \times 100\% \\
 &= 86.957\% \\
 &\approx \mathbf{87.0\%}
 \end{aligned}$$

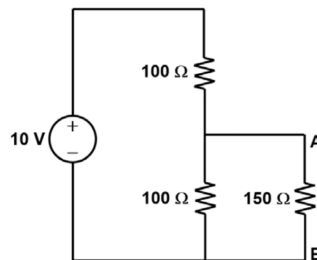2. The figure below shows a **loaded** voltage divider circuit. Calculate the voltage difference  $V_{AB}$  (given by  $V_A - V_B$ ):




**Solution:**

$$\begin{aligned}
 R_{AB} &= \left( \frac{1}{100} + \frac{1}{150} \right)^{-1} \\
 &= 60 \text{ } \Omega \\
 R_{\text{eff}} &= 100 + 60 = 160 \text{ } \Omega \\
 I_g &= \frac{\varepsilon}{R_{\text{eff}}} \\
 &= \frac{10}{160} \\
 &= 0.0625 \text{ A} \\
 V_{AB} &= I_g \times R_{AB} \\
 &= 0.0625 \times 60 \\
 &= \mathbf{3.75 \text{ V}}
 \end{aligned}$$

3. Considering the circuit diagram shown in the figure below, which of the following


correctly applies **both** KVL and KCL?

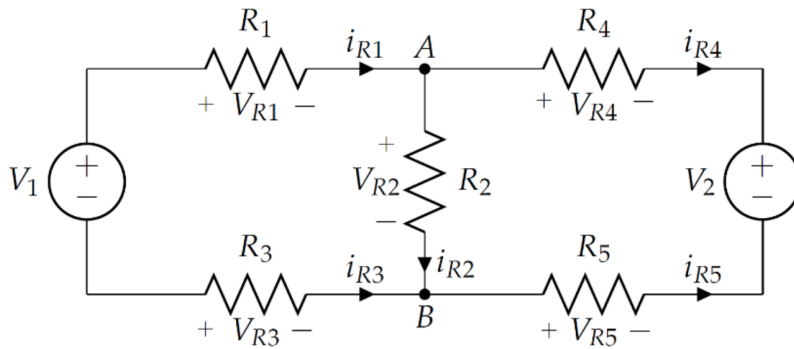

- A.  $V_1 - V_{R1} - V_{R2} - V_{R3} = 0$ ;  $i_{R1} - i_{R2} - i_{R4} = 0$
- B.  $V_1 + V_{R3} - V_{R1} - V_{R2} = 0$ ;  $i_{R1} + i_{R3} = 0$
- C.  $V_2 + V_{R4} + V_{R2} + V_{R5} = 0$ ;  $i_{R4} + i_{R5} = 0$
- D.  $V_2 + V_{R4} - V_{R2} - V_{R5} = 0$ ;  $i_{R3} - i_{R2} - i_{R5} = 0$

**Solution: D**

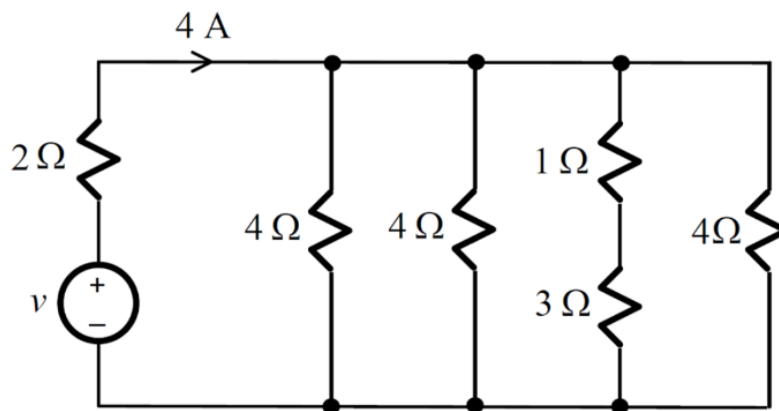4. Determine the source voltage  $v$  and the voltage across the  $3\ \Omega$  resistor in the following circuit.



**Solution:**

$$R_{//} = \left(3 \times \frac{1}{4} + \frac{1}{3+1}\right)^{-1}$$

$$= 1 \, \Omega$$

$$v = I_g R_{\text{eff}}$$

$$= (4) \times (2+1)$$

$$= \mathbf{12 \, V}$$


$$V_{//} = I_g \times R_{//}$$

$$= 4 \times 1 = 4 \, \text{V}$$

$$V_{3\, \Omega} = V_{//} \times \frac{3}{3+1}$$

$$= \mathbf{3 \, V}$$

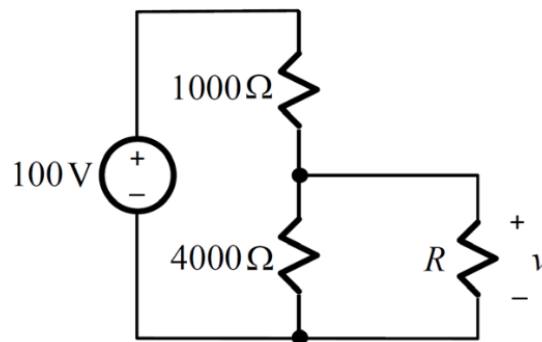5. The following circuit shows a common voltage divider for obtaining a certain voltage  $v$  across a load resistor  $R$ .



A novice may forget to include the loading effects of  $R$ . To understand these effects, determine  $v$  and the current in  $R$ ,  $I_R$  when

- (a)  $R = \infty$  (open circuit)

**Solution:**

$$R_{//} = \left(\frac{1}{4000} + \frac{1}{\infty}\right)^{-1}$$

$$= 4000 \, \Omega$$

$$V_{//} = \varepsilon \times \frac{4000}{4000 + 1000}$$

$$v = 100 \times 0.8$$

$$= \mathbf{80 \, V}$$

$$I_R = \mathbf{0 \, A}$$

- (b)  $R = 8000 \, \Omega$

**Solution:**

$$R_{//} = \left( \frac{1}{4000} + \frac{1}{8000} \right)^{-1}$$
$$= \frac{8000}{3} \, \Omega$$

$$V_{//} = \varepsilon \times \frac{\frac{8000}{3}}{\frac{8000}{3} + 1000}$$

$$v = 100 \times \frac{8}{11}$$

$$= 72.72727$$

$$\approx \mathbf{72.7 \, V}$$

$$I_R = \frac{v}{R}$$

$$= \frac{72.72727}{8000}$$

$$= 9.0909 \times 10^{-3} \, \text{A}$$

$$\approx \mathbf{9.09 \, \text{mA}}$$

(c)  $R = 200 \, \Omega$

**Solution:**

$$R_{//} = \left( \frac{1}{4000} + \frac{1}{200} \right)^{-1}$$
$$= \frac{4000}{21} \, \Omega$$

$$V_{//} = \varepsilon \times \frac{\frac{4000}{21}}{\frac{4000}{21} + 1000}$$

$$v = 100 \times \frac{4}{25}$$

$$= \mathbf{16 \, V}$$

$$I_R = \frac{v}{R}$$

$$= \frac{16}{200}$$

$$= 0.08 \, \text{A}$$

$$= \mathbf{80 \, \text{mA}}$$

(d)  $R = 0$  (short circuit)

**Solution:**

$$R_{//} = \left( \frac{1}{4000} + \frac{1}{0} \right)^{-1}$$

$$= 0 \, \Omega$$

$$V_{//} = \varepsilon \times \frac{0}{0 + 1000}$$

$$= 0 \, \text{V}$$


$$I_R = \frac{\varepsilon - V_{//}}{1000}$$

$$= \frac{100}{1000}$$

$$= 0.1 \, \text{A}$$

$$= 100 \, \text{mA}$$

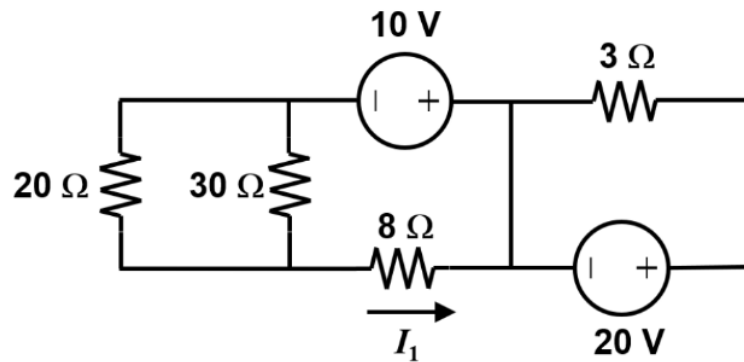6. For the circuit shown in the figure below, what is the value of current  $I_1$ ?



**Solution:**

Notice that due to the single wire, the 20 V source and the 3 Ω resistor are in a separate circuit altogether. Thus, we only need to simply apply Ohm's Law as follows:


$$R_{//} = \left( \frac{1}{20} + \frac{1}{30} \right)^{-1} = 12 \, \Omega$$

$$I = \frac{\varepsilon}{R_{\text{eff}}}$$

$$-I_1 = \frac{10}{12 + 8}$$

$$I_1 = -0.5 \, \text{A}$$

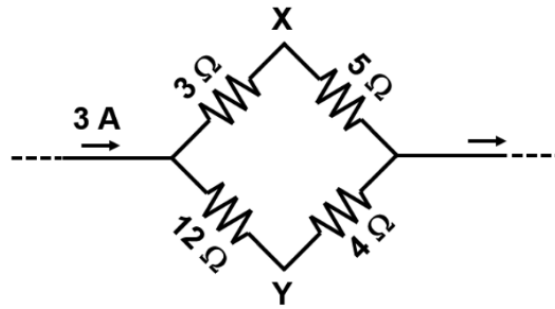7. A current of 3 A flows through a resistor network as shown in the figure below. What is the voltage difference  $V_{XY}$  (given by  $V_X - V_Y$ )?



**Solution:**

Denoting the one above as branch 1, and the one below as branch 2,

$$R_{//} = \left( \frac{1}{3+5} + \frac{1}{12+4} \right)^{-1} = \frac{16}{3} \, \Omega$$

$$I_1 = I \times \frac{R_{//}}{R_1} = 3 \times \frac{\frac{16}{3}}{3+5} = 2 \, \text{A}$$


$$I_2 = I \times \frac{R_{//}}{R_2} = 3 \times \frac{\frac{16}{3}}{12+4} = 1 \, \text{A}$$

$$V_{3 \, \Omega} = I_1 \times 2 = -6 \, \text{V}$$

$$V_{12 \, \Omega} = I_2 \times 1 = -12 \, \text{V}$$

$$\begin{aligned} V_{XY} &= -6 - (-12) \\ &= 6 \, \text{V} \end{aligned}$$

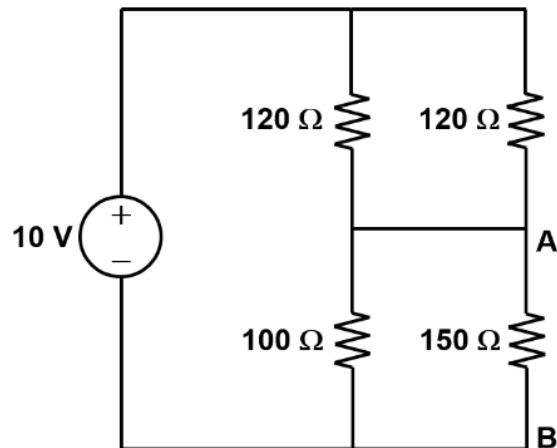8. What is the voltage difference  $V_{AB}$  (given  $V_A - V_B$ )?



**Solution:**

This is effectively two parallel sets in series, which can be denoted as  $//1$  and  $//2$ :


$$R_{//1} = (2 \times \frac{1}{120})^{-1} = 60 \, \Omega$$

$$R_{//2} = (\frac{1}{100} + \frac{1}{150})^{-1} = 60 \, \Omega$$

$$V_{//2} = \varepsilon \times \frac{R_{//2}}{R_{//2} + R_{//1}}$$

$$V_{AB} = 10 \times \frac{1}{2} \\ = 5 \, \text{V}$$

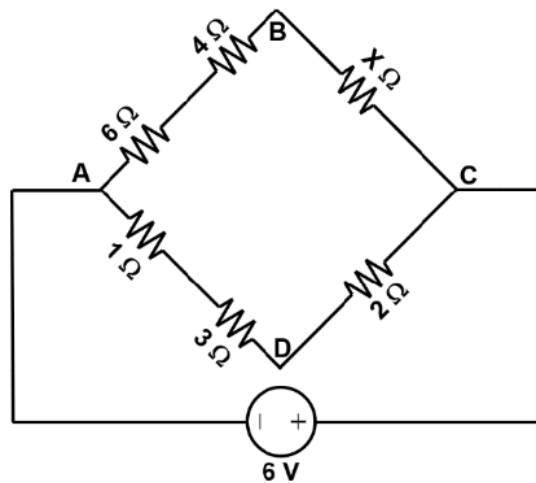9. For the circuit shown in the figure below, if the voltage difference  $V_{BD}$  (given by  $V_B - V_D$ ) is 1 V, what is the value of resistance X?





**Solution:**

Denoting the one above as branch 1, and the one below as branch 2,

$$I_1 = \frac{\varepsilon}{6 + 4 + X} = \frac{6}{10 + X}$$

$$I_2 = \frac{\varepsilon}{1 + 3 + 2} = 1$$

$$V_X = -I_1 \times X = -\frac{6X}{10 + X}$$

$$V_{2\Omega} = -I_2 \times 2 = -2$$

$$V_{BD} = 2 - \frac{6X}{10 + X}$$

$$1 \text{ V} = 2 - \frac{6X}{10 + X}$$


$$\frac{6X}{10 + X} = 1$$

$$6X = 10 + X$$

$$5X = 10$$

$$X = \mathbf{2\ \Omega}$$

10. The circuit below shows a  $10\ \Omega$  load connected to three batteries in parallel. Using node voltage analysis method, determine the voltage across the  $10\ \Omega$  load,  $V$ , and its current  $i$ .

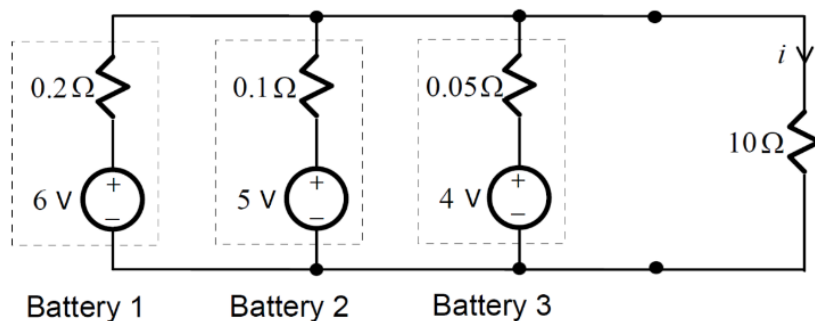**Solution:**

Ground the bottom wire. Denote Voltage of top wire as  $V$ .

$$\frac{6 - V}{0.2} + \frac{5 - V}{0.1} + \frac{4 - V}{0.05} = \frac{V}{10}$$


$$300 - 50V + 500 - 100V + 800 - 200V = V$$

$$351V = 1600$$

$$V = 4.55840 \approx \mathbf{4.56\ V}$$

$$i = \frac{V}{10} \approx \mathbf{0.456\ A}$$

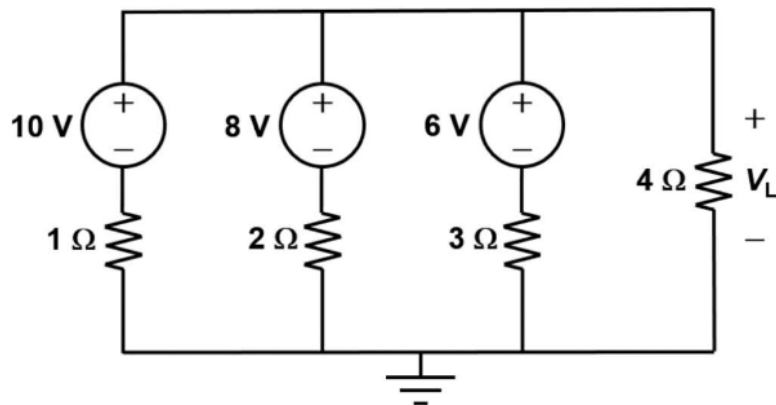11. For the circuit shown in the figure below, what is the voltage  $V_L$ ? (*Hint: Use Node Voltage Analysis method*) How much power is the 6V source supplying/consuming?




**Solution:**

$$\begin{aligned}\frac{10 - V_L}{1} + \frac{8 - V_L}{2} + \frac{6 - V_L}{3} &= \frac{V_L}{4} \\ 120 - 12V_L + 48 - 6V_L + 24 - 4V_L &= 3V_L \\ 25V_L &= 192 \\ V_L &= \mathbf{7.68 \text{ V}} \\ I_{6\text{V}} &= \frac{6 - V_L}{3} = -0.56 \text{ A} \\ P &= IV = -0.56 \times 6 \\ &= \mathbf{-3.36 \text{ W}}\end{aligned}$$

Thus it is consuming **3.36 W** of power.

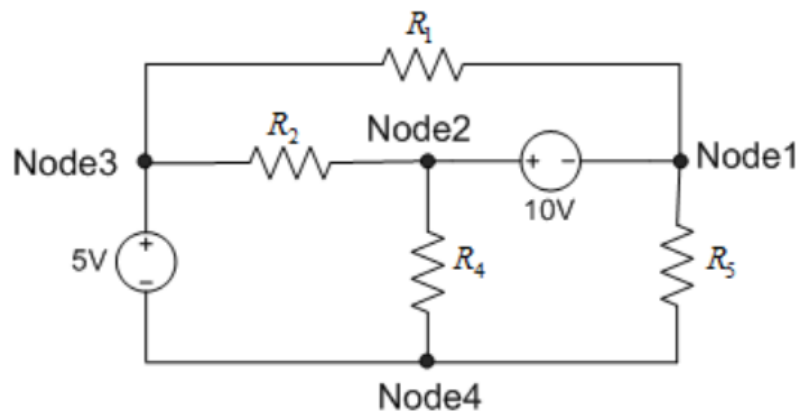12. Consider the circuit given below. Suppose  $R_5$  is the load resistance, derive and draw the Thevenin equivalent circuit as seen by  $R_5$ . clearly labeling Node 1 and Node 4 in the equivalent circuit. (Assume that  $R_1 = 1 \Omega$ ,  $R_2 = 2 \Omega$ ,  $R_4 = 1 \Omega$ )



**Solution:** NO.