


Alternating Current Studio Report

CG1111A Studio 6


Prannaya Gupta (B02)

August 31, 2022


0.1 Setting Up

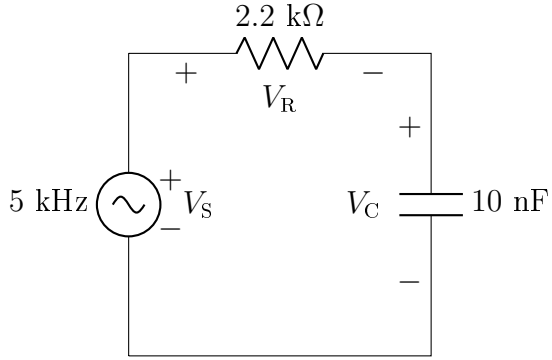

(a) The Circuit Set-Up

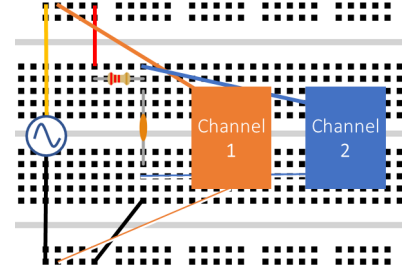

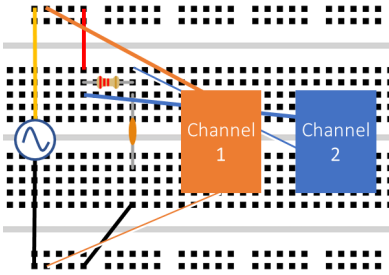(b) The Circuit Wiring (including AD2) for V_C



(c) The Circuit Wiring (including AD2) for V_R

Figure 1: Final Set-Up Utilized

The measured resistance of the resistor is **2.16 k Ω** .

	Amplitude, V_o (V)	RMS (V)	Measured ΔT (μ S)	Leading or lagging V_S ?	Calculated phase angle, ϕ (degrees)	Phasor (Amplitude \angle Phase Angle)
V_S	3.0216	2.1391	—	—		$3.02\angle 0^\circ$
V_C	2.3122	1.6349	19.518	lagging	-35.0238	$2.31\angle -35.0^\circ$
V_R	1.7195	1.2262	-28.042	leading	50.6946	$1.72\angle 50.7^\circ$

0.2 Results

0.2.1 Why KVL cannot be applied on RMS Voltage

$$\begin{aligned} V_C + V_R &= 2.3122 + 1.7195 \\ &= 4.0317 \text{ V} \neq V_S \end{aligned}$$

This is likely due to the fact that over the period of the waveform, the Voltage and Current are clearly constantly changing and hence at different points, the impedance is different. Thus, KVL cannot be applied overall since the changing impedances don't add up together to work hand-in-hand in this scenario. KVL applies for instantaneous conditions, whereas the RMS value is in fact the average value.

0.2.2 Verifying KVL in terms of Phasors

$$\begin{aligned} V_R + V_C &= V_{o, R} \angle \phi_R + V_{o, C} \angle \phi_C \\ &= V_{o, R} \cos \phi_R + V_{o, C} \cos \phi_C \\ &= 1.7195 \cos(50.6946) + 2.3122 \cos(-35.0238) \\ &= 2.9827 \cong 3.0126 \end{aligned}$$

Thus, KVL does in fact work in the phasor space.

0.2.3 Phasor Diagram

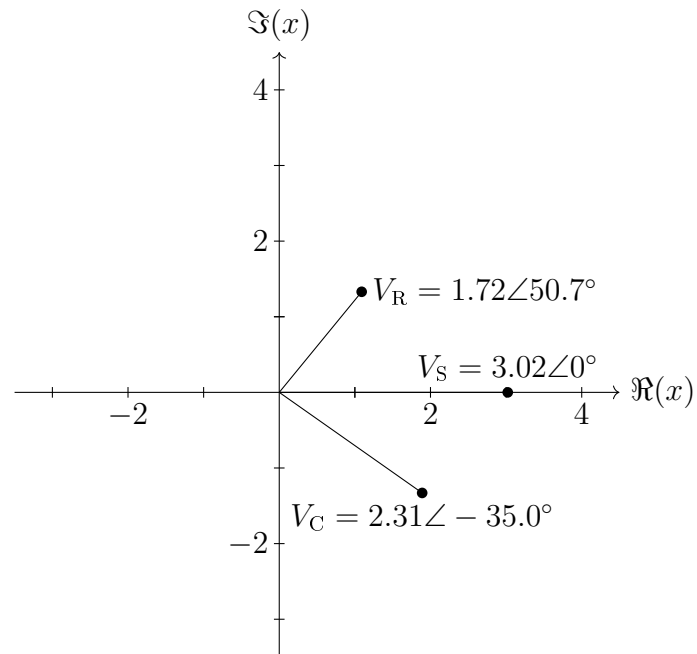


Figure 2: Phasor Diagram for Activity 1

0.3 Evaluation

0.3.1 Phasor for I_S

$$\begin{aligned}
 \tilde{I}_S &= \frac{\tilde{V}_R}{R} \\
 &= \frac{1.72 \angle 50.6946^\circ}{2.16 \times 10^3} \\
 &= 0.78182 \angle 50.6946^\circ \text{ mA}
 \end{aligned}$$

0.3.2 Z_C in terms of C

$$\begin{aligned} Z_C &= \frac{1}{j\omega C} \\ &= -\frac{j}{(100\pi \times 10^3)C} \\ &= -\frac{j}{(31415.92654)C} \end{aligned}$$

0.3.3 Estimate of C

$$\begin{aligned} Z_C &= \frac{\tilde{V}_C}{\tilde{I}_S} \\ \frac{1}{j(314159.2654)C} &= \frac{2.3122 \angle -35.0238^\circ}{0.78182 \angle 50.6946^\circ \times 10^{-3}} \\ C &= \frac{0.78182 \angle 50.6946^\circ \times 10^{-3}}{31415.92654 \times (2.3122 \angle 54.9762^\circ)} \\ &= 10.73292 \text{ nF} \approx \mathbf{10.7 \text{ nF}} \end{aligned}$$

0.3.4 Two Possible Sources of Experimental Errors

- The wires may contain resistance which causes the distribution of phasor voltage to be slightly disproportionate.
- The capacitor has non-zero resistance which can also cause said disproportionate distribution of phasor voltage.