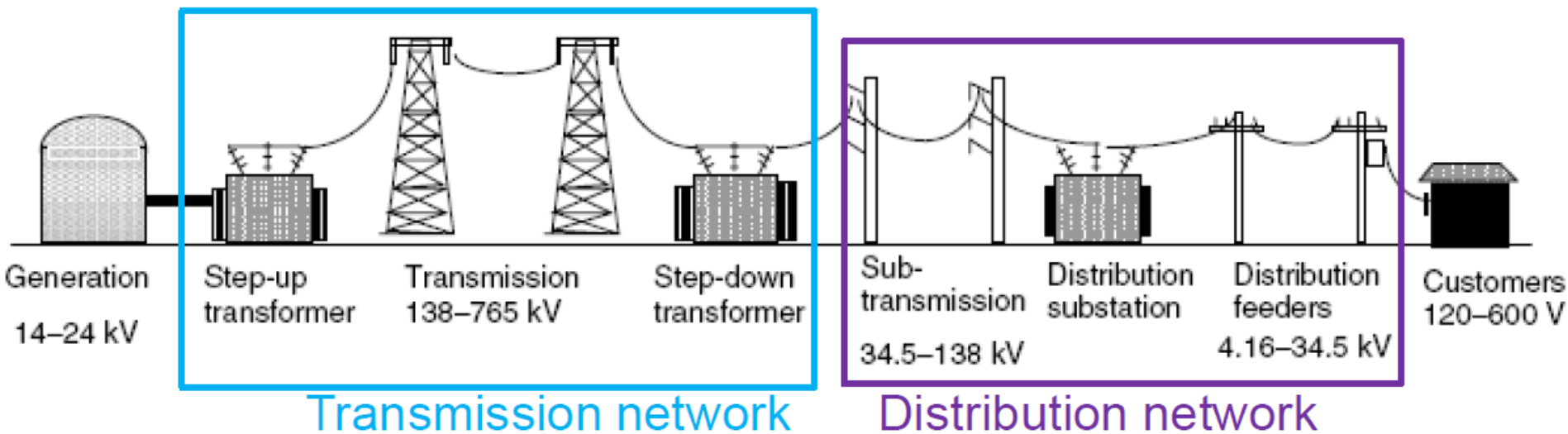


CG1111A: Engineering Principles & Practice I

Tutorial 3: Reflections & Problem Solutions
(28/29 Sep 2022)



Why Transformers?




- More efficient if electricity transmitted at very high voltage:
 - For the **same power P** , higher $V \rightarrow$ smaller I
 - Smaller $I \rightarrow$ smaller power loss (Recall that $P = I^2 R$)
 - Smaller $I \rightarrow$ can use thinner transmission lines

Example


Transmitted Power	Source Voltage	Current	Transmission Line's Resistance	Power Loss in Transmission Line (I^2R)
1 MW	100 kV	10 A	1 Ω	100 W
1 MW	10 kV	100 A	1 Ω	10000 W = 10 kW
1 MW	10 kV	100 A	0.01 Ω	100 W

Recall that $R = \frac{\rho l}{A}$

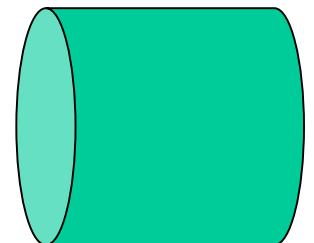If **V decreases** by **10x**, you need to **increase wire thickness** by **100x** to maintain the same low power loss!




Step-Up/Down Transformer

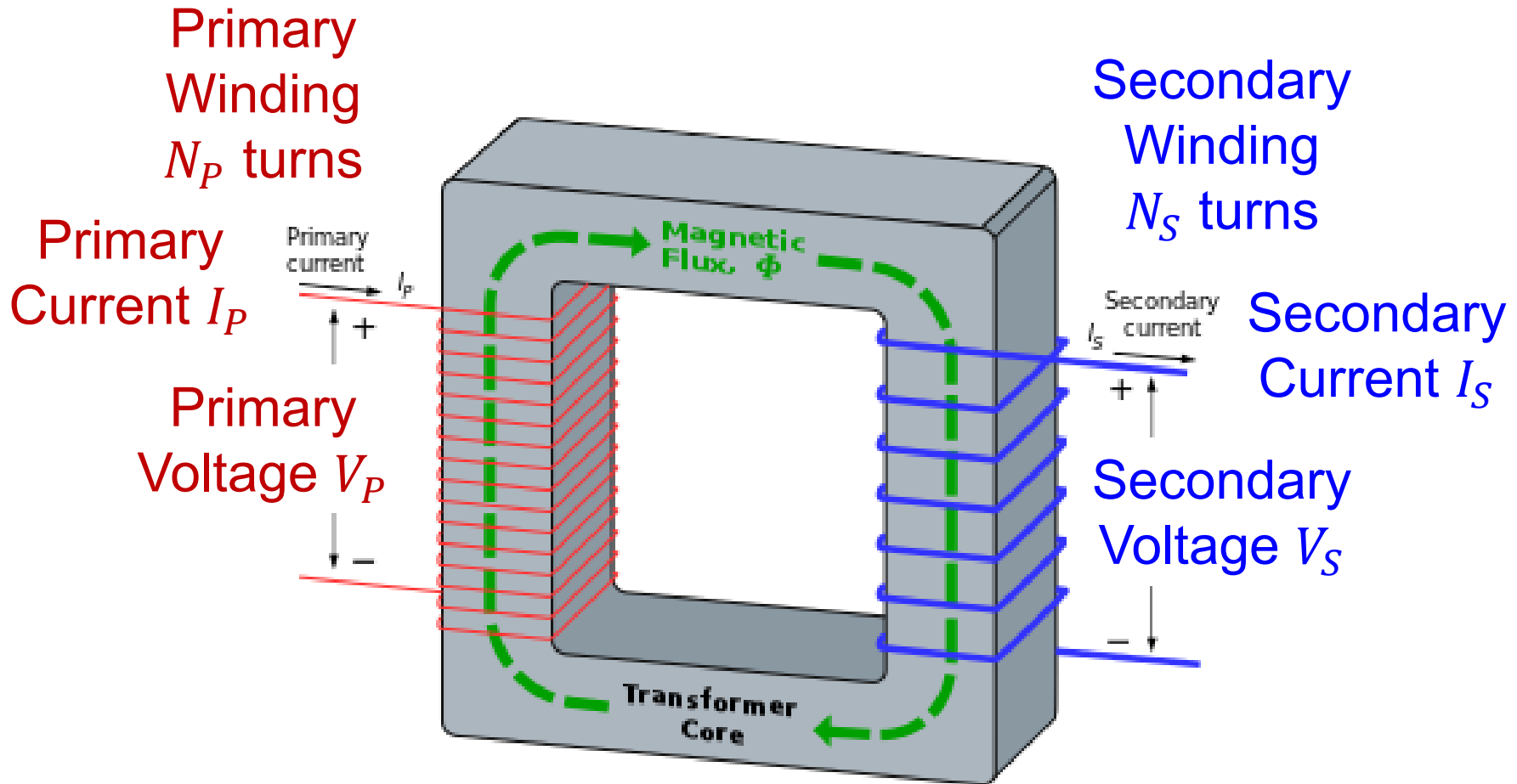



$$\frac{V_S}{V_P} = \frac{N_S}{N_P}$$

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}$$

Why Rectifier?

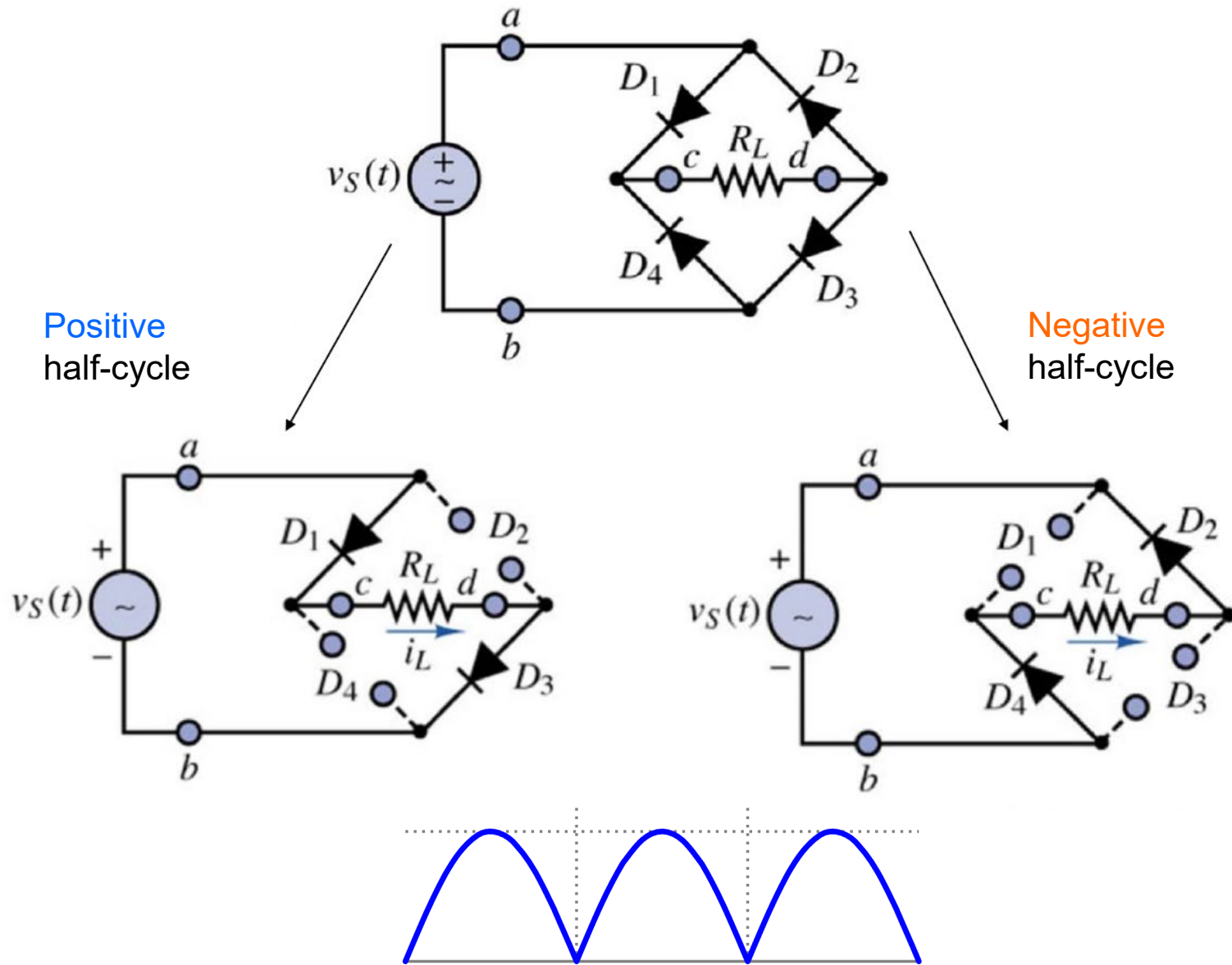

Why Filter Capacitor?

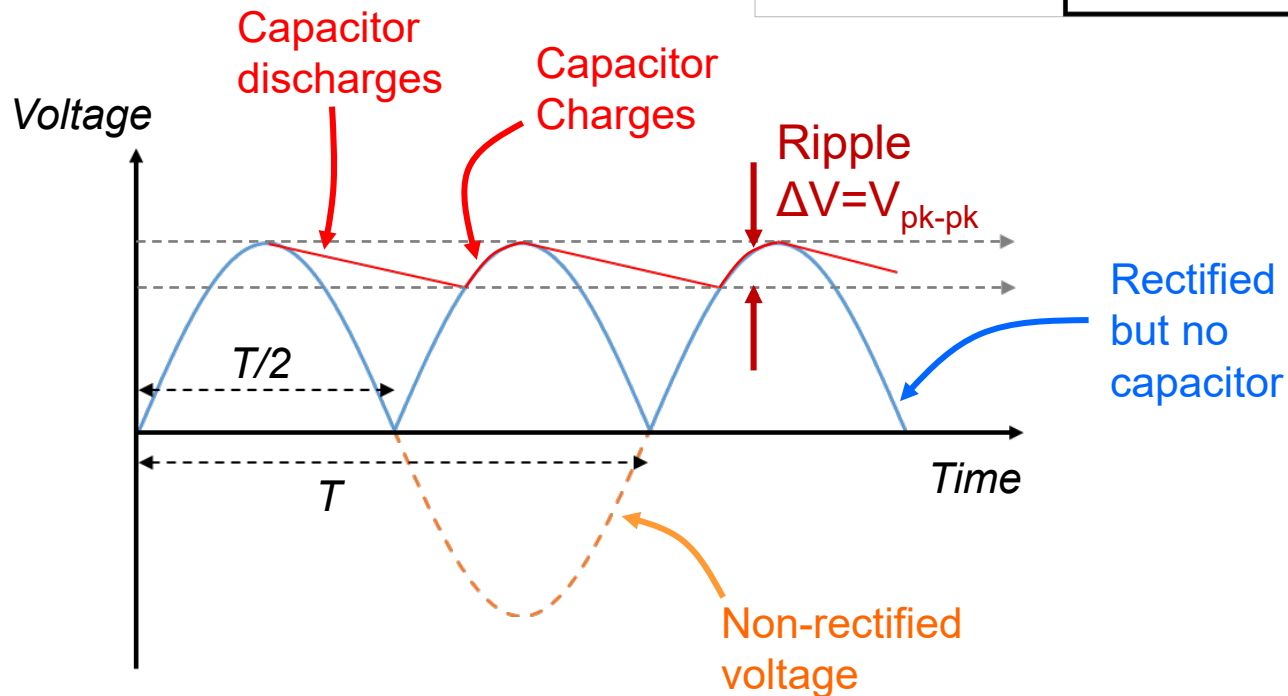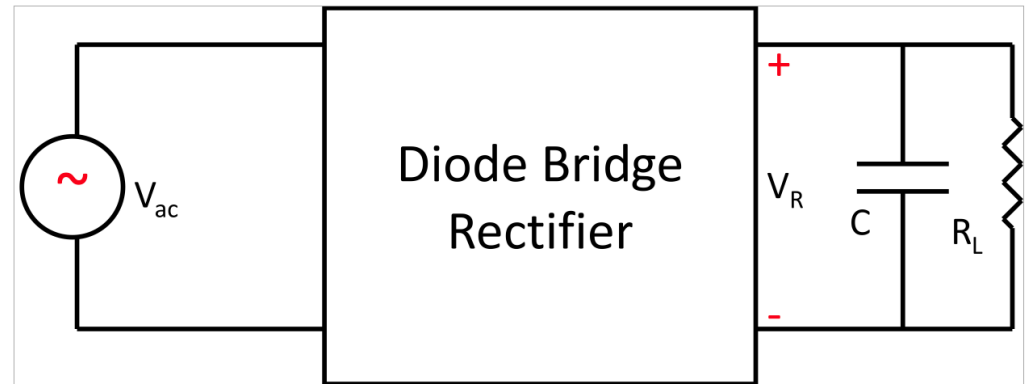

Characteristics of DC Motors

Torque of shaft:

$$T_{\text{shaft}} = K_t I_m \text{ [N.m]}$$

Back emf:

$$E_b = K_e \omega \text{ [V]}$$

For PMDC motor:

$$K_t = K_e$$

Note:

$$\omega = 2\pi \times \frac{\text{RPM}}{60} \text{ [rad/s]}$$


Power Conversion in Motors

- Mechanical power at motor shaft:


$$P_{\text{mech}} = T_{\text{shaft}} \omega \text{ [W]}$$

- Electrical power supplied to motor:

$$P_{\text{in}} = V_m I_m \text{ [W]}$$

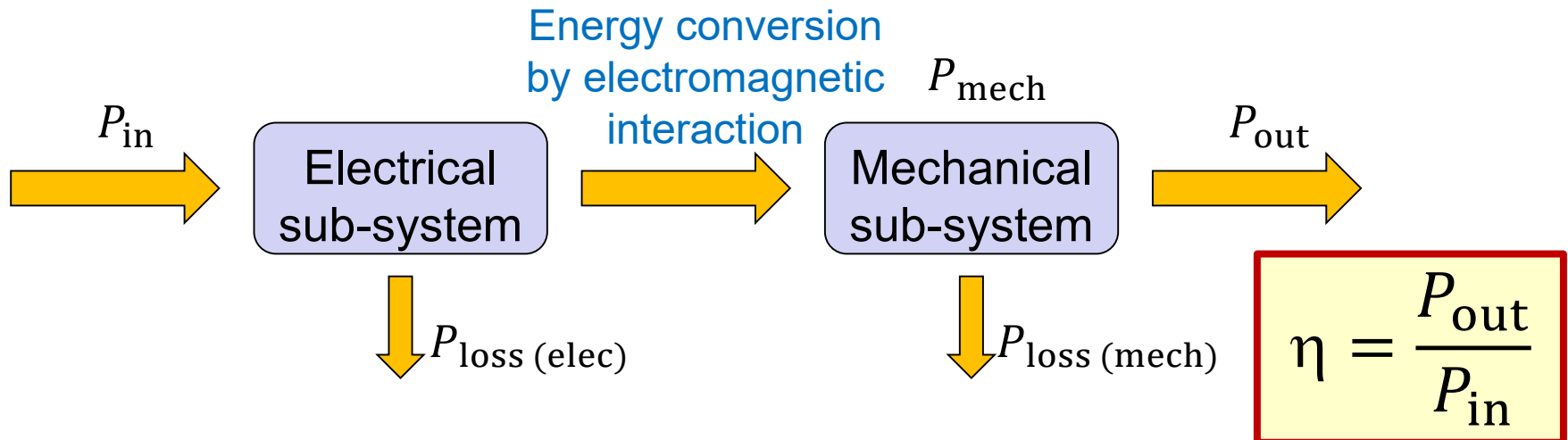

Circuit Representation: PMDC Motor

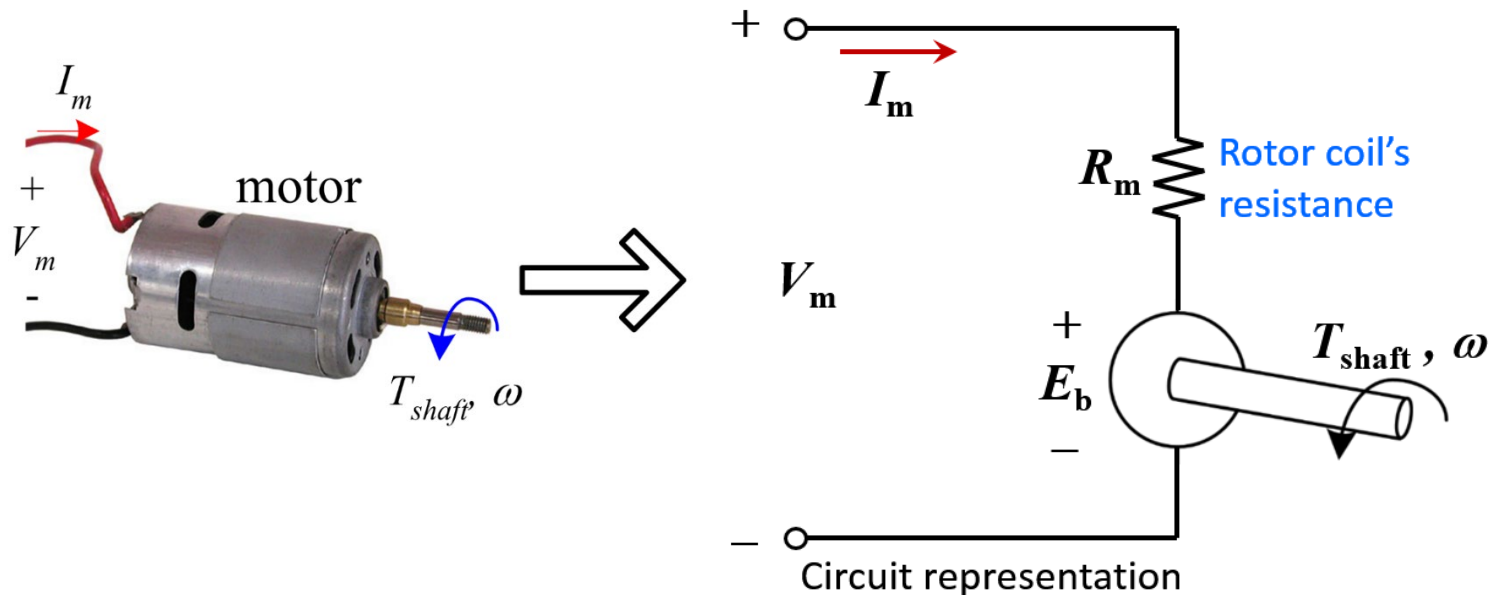

- From the circuit:
$$I_m = \frac{V_m - E_b}{R_m}$$

- Since $E_b = K_e \omega$, we have:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

Basic Properties of PMDC Motor

Rearranging:

$$\omega = \frac{V_m}{K_e} - \frac{R_m I_m}{K_e}$$

- For a **fixed load** (i.e., **fixed** T_{shaft} , which implies **fixed** I_m since $T_{\text{shaft}} = K_t I_m$):


Shaft speed ω can be increased by increasing motor voltage V_m

- For a **fixed voltage**, if T_{shaft} increases, I_m increases, and hence ω decreases:

Shaft speed ω decreases with increasing load T_{shaft}

What is an “Operational Amplifier”?

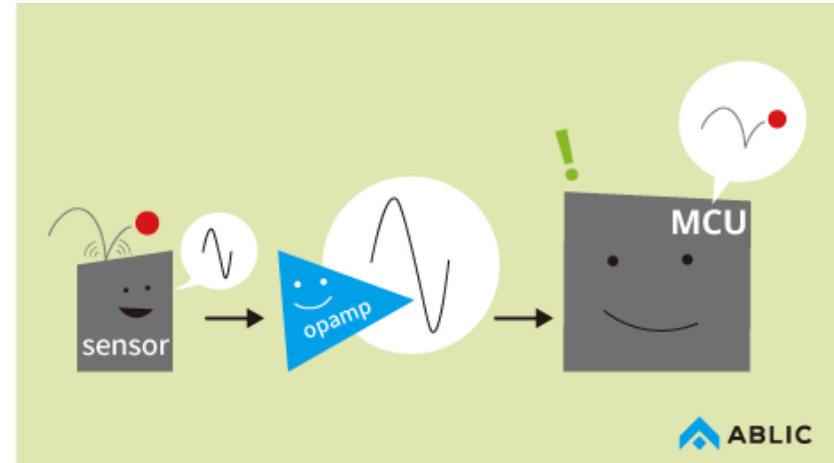- An “operational amplifier (**op-amp**)” is an integrated circuit that can amplify weak electric signals




Credit: Image from ablic.com

- It has **two input** signal terminals and **one output** signal terminal
- It amplifies and outputs the **voltage difference** between the two input terminals


The Need for Amplifying Signals

- Voltage output from sensors may be in the order of **mV**, e.g., microphone signals
- The sensor voltage output would need to be scaled before A-to-D conversion for more accurate measurements (e.g., using Arduino Uno)

Op-Amp Terminals

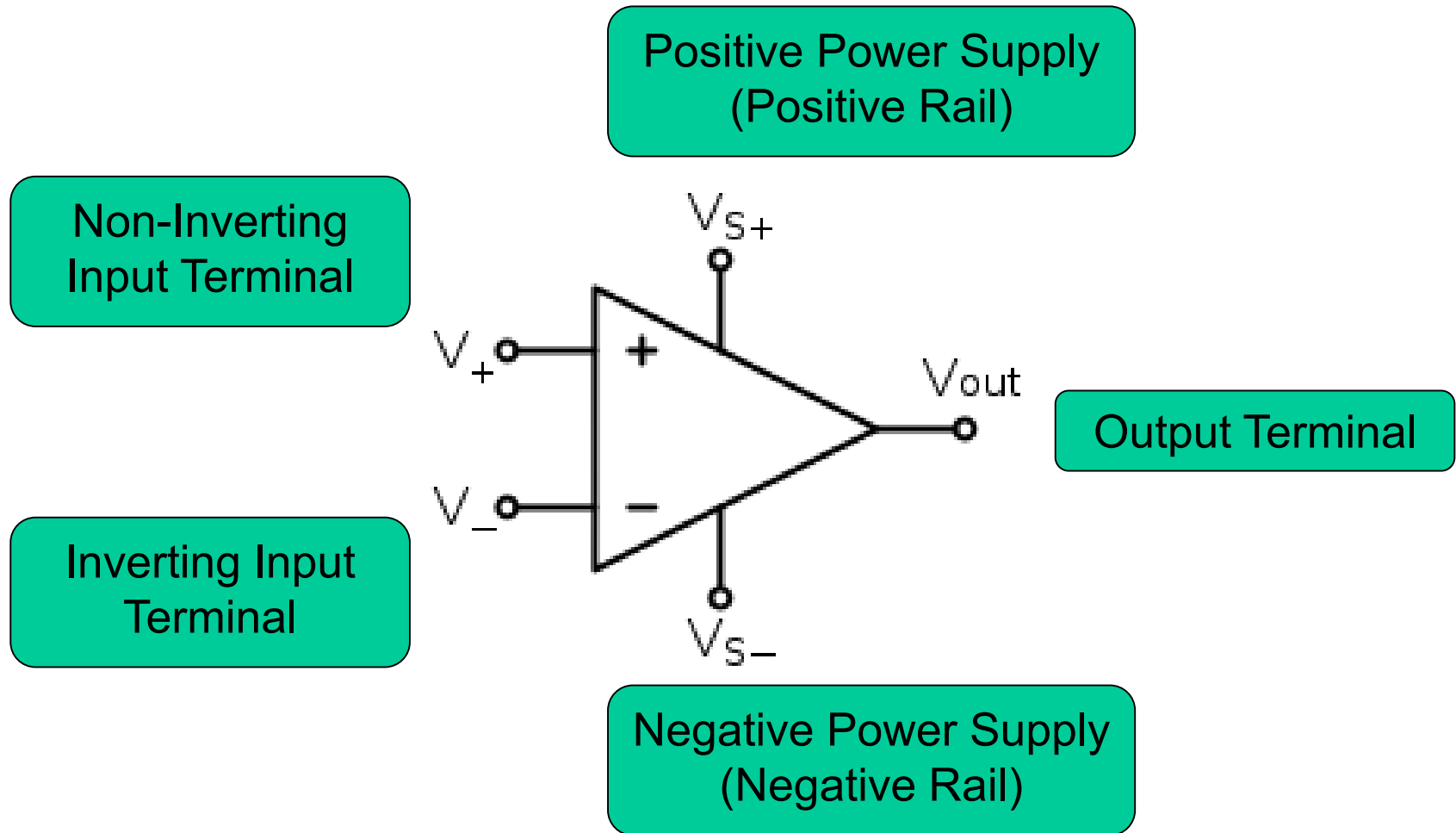


Op-Amp Equivalent Circuit

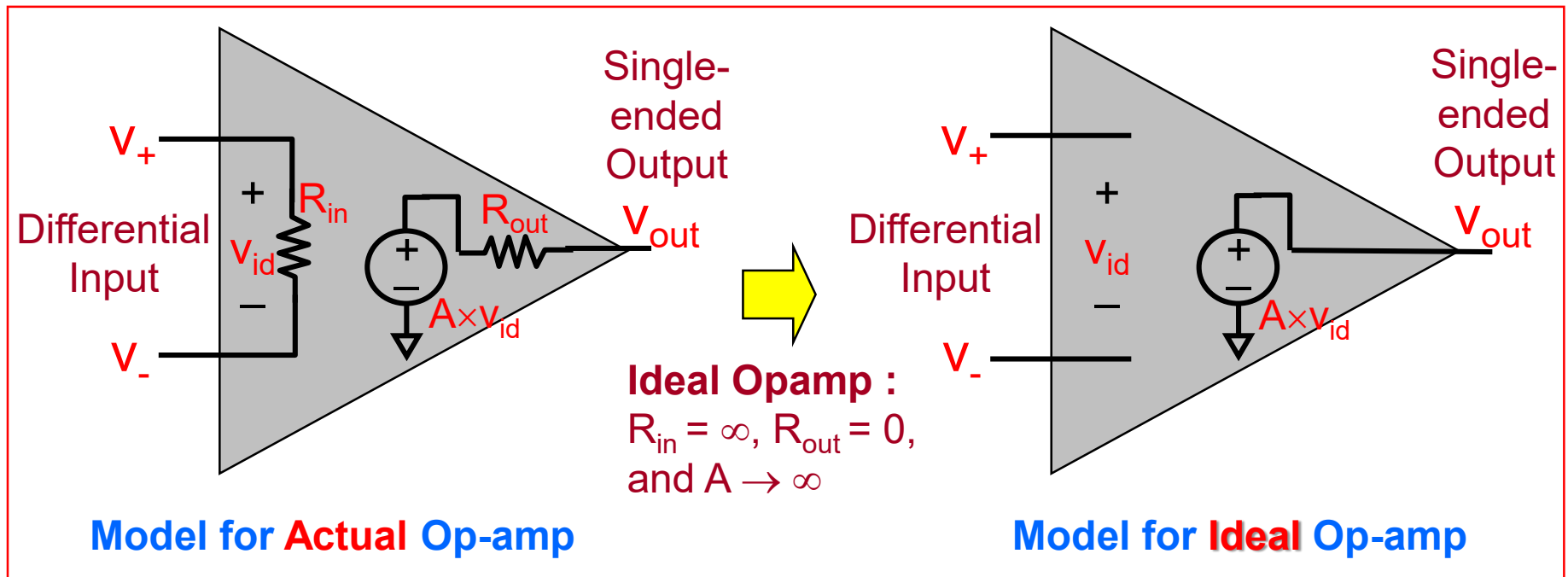

- **A** is the open-loop voltage gain
– It is very large, approaching infinity
- **R_{in}** is the input impedance (very large) & **R_{out}** is the output impedance (very small)
- To **simplify** analysis, we always assume **infinite R_{in}** and **A** , and **zero R_{out}**

Op-amp's Saturation Voltage

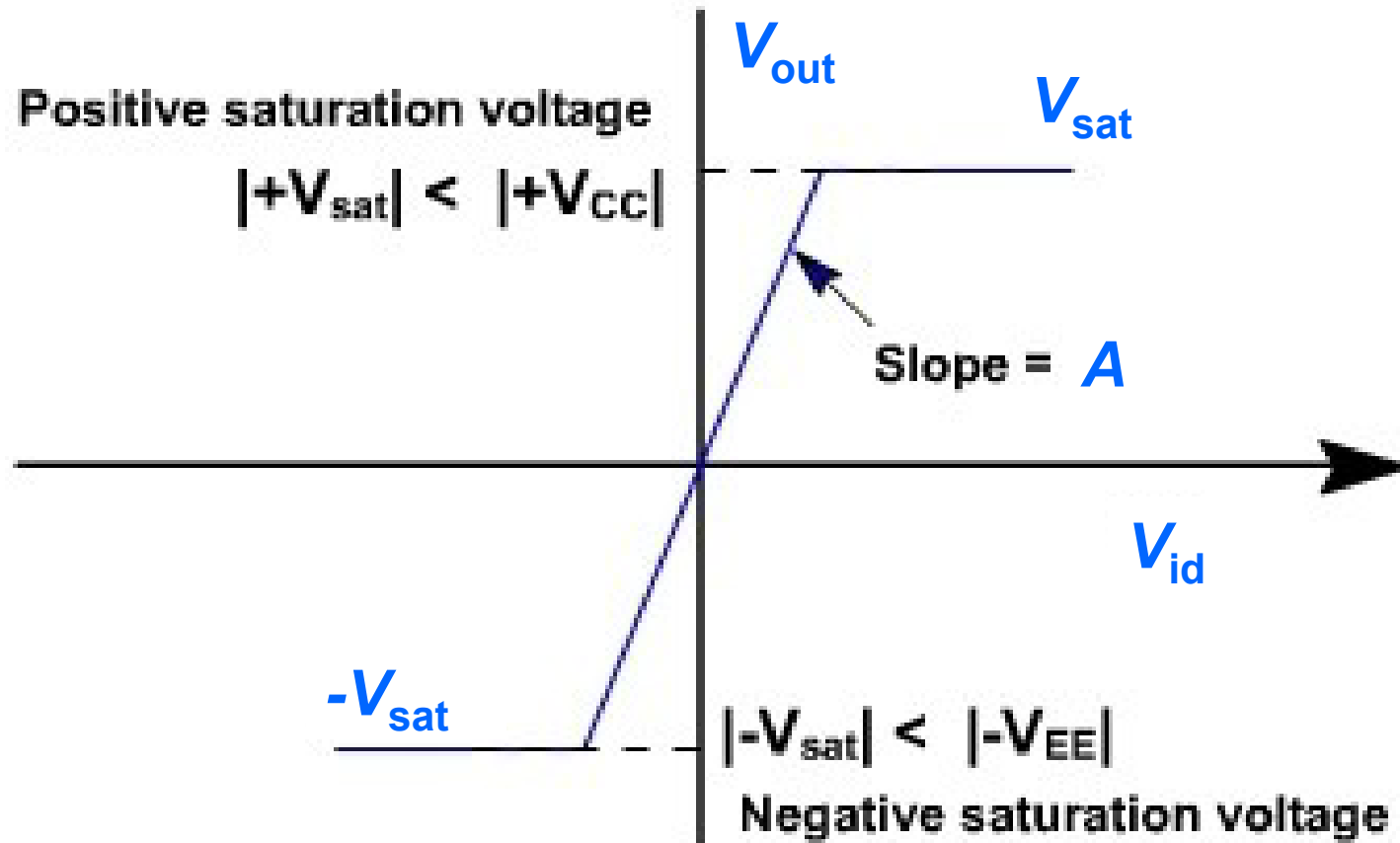

Typical Op Amp Parameters

Parameter	Variable	Typical Ranges	Ideal Values
Voltage Gain	A	10^5 to 10^8	∞
Input Impedance	R_{in}	10^5 to $10^8 \Omega$	$\infty \Omega$
Output Impedance	R_{out}	10s to 100s Ω	0Ω
Supply Voltage	V_S $-V_S$	3 to 30 V -30 to 0 V	N/A N/A

Op-amp Golden Rules


- Rule 1: In a closed loop with -ve feedback, the output attempts to do whatever is necessary to make the voltage difference between the inputs zero

- The voltage gain of a real op-amp is so high that a fraction of a mV difference between the V_+ & V_- inputs will achieve the desired finite output


- “Virtual short”, i.e., $V_+ \approx V_-$

- Rule 2: The inputs draw no current

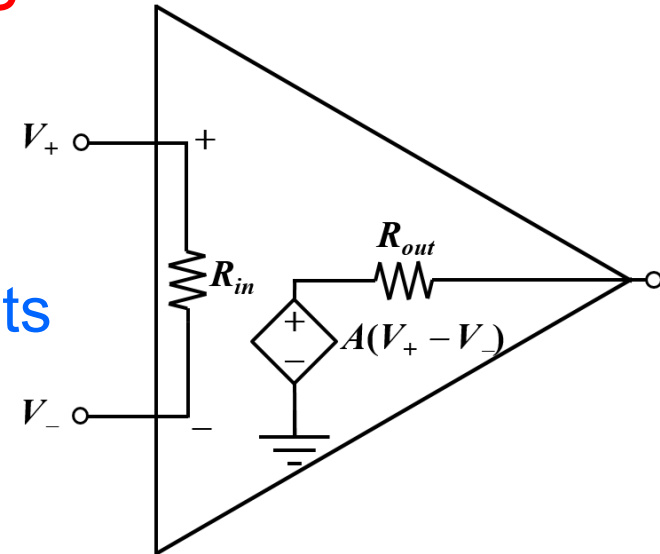
- The ideal op-amp has very large input impedance (R_{in}). Thus, the current drawn at the two input terminals ~ 0 .



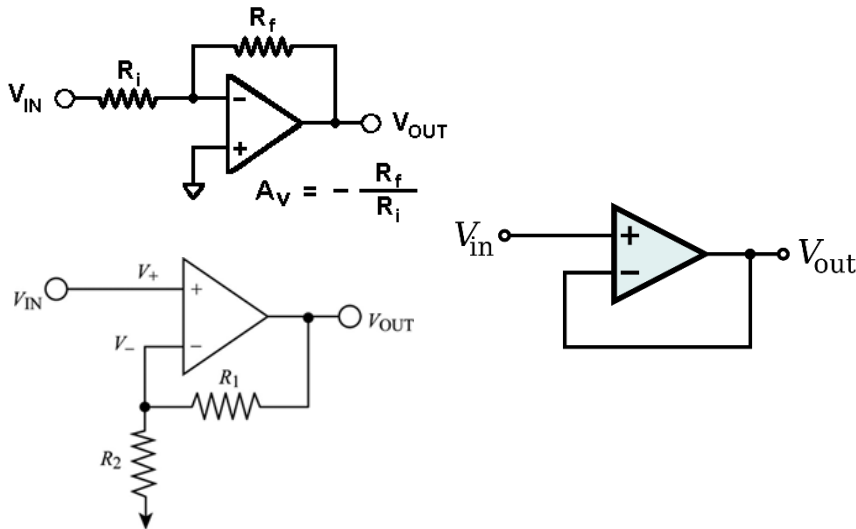What is Closed Loop with Negative Feedback?




Negative Feedback

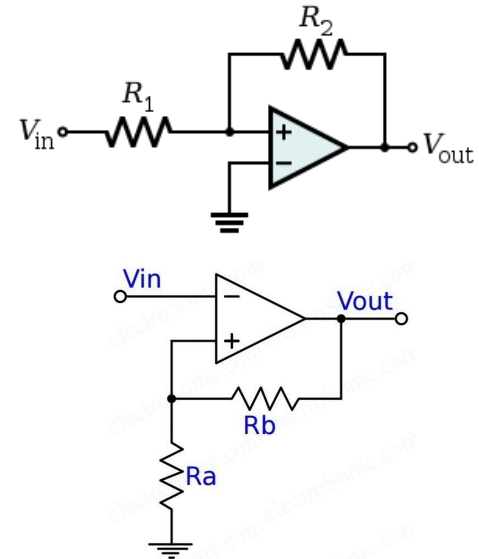

Positive Feedback

- **Closed loop:** There is connection between output and input
- **Negative feedback:** The output is fed back to the input in such a way to **reduce** the **output fluctuations**

Inverting Amplifier

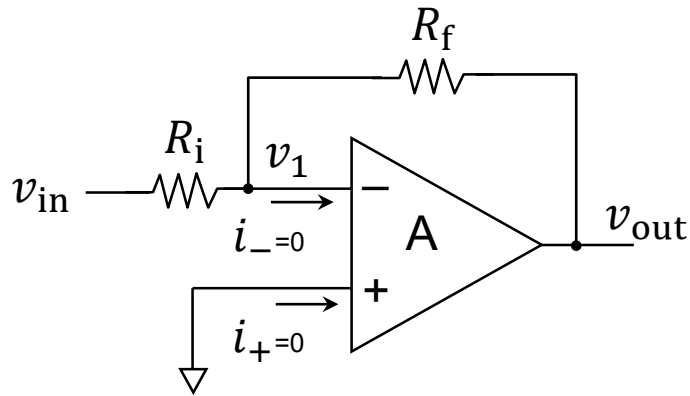

$$\frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$


Derivation based on Golden Rules

$$v_1 = v_- \approx v_+ = 0 \quad [\because \text{Virtual Short}]$$

$$\frac{v_{\text{in}} - v_1}{R_i} = \frac{v_1 - v_{\text{out}}}{R_f} \quad [\because i_- \approx 0]$$

$$\Rightarrow \frac{v_{\text{in}}}{R_i} = \frac{-v_{\text{out}}}{R_f} \Rightarrow \frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$

Non-Inverting Amplifier

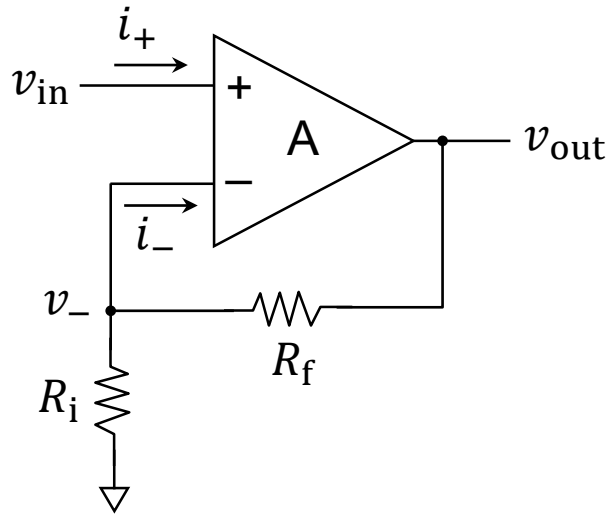

$$\frac{v_{\text{out}}}{v_{\text{in}}} = 1 + \frac{R_f}{R_i}$$


Derivation based on Golden Rules

$$v_- \approx v_+ = v_{\text{in}} \quad [\because \text{Virtual Short}]$$

$$v_- = v_{\text{out}} \times \frac{R_i}{R_i + R_f} \approx v_{\text{in}} \quad [\because i_- \approx 0]$$

$$\Rightarrow \frac{v_{\text{out}}}{v_{\text{in}}} = \left(1 + \frac{R_f}{R_i} \right)$$


Significance of Ratio

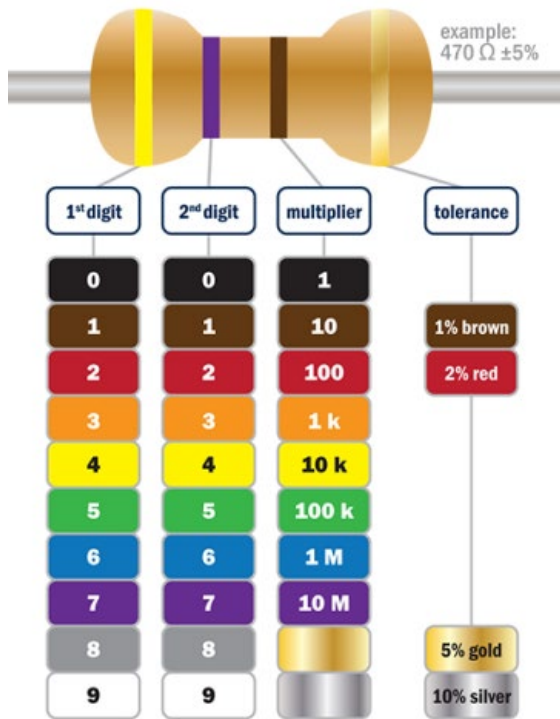

$$\frac{v_{\text{out}}}{v_{\text{in}}} = -\frac{R_f}{R_i}$$

$$\frac{v_{\text{out}}}{v_{\text{in}}} = 1 + \frac{R_f}{R_i}$$

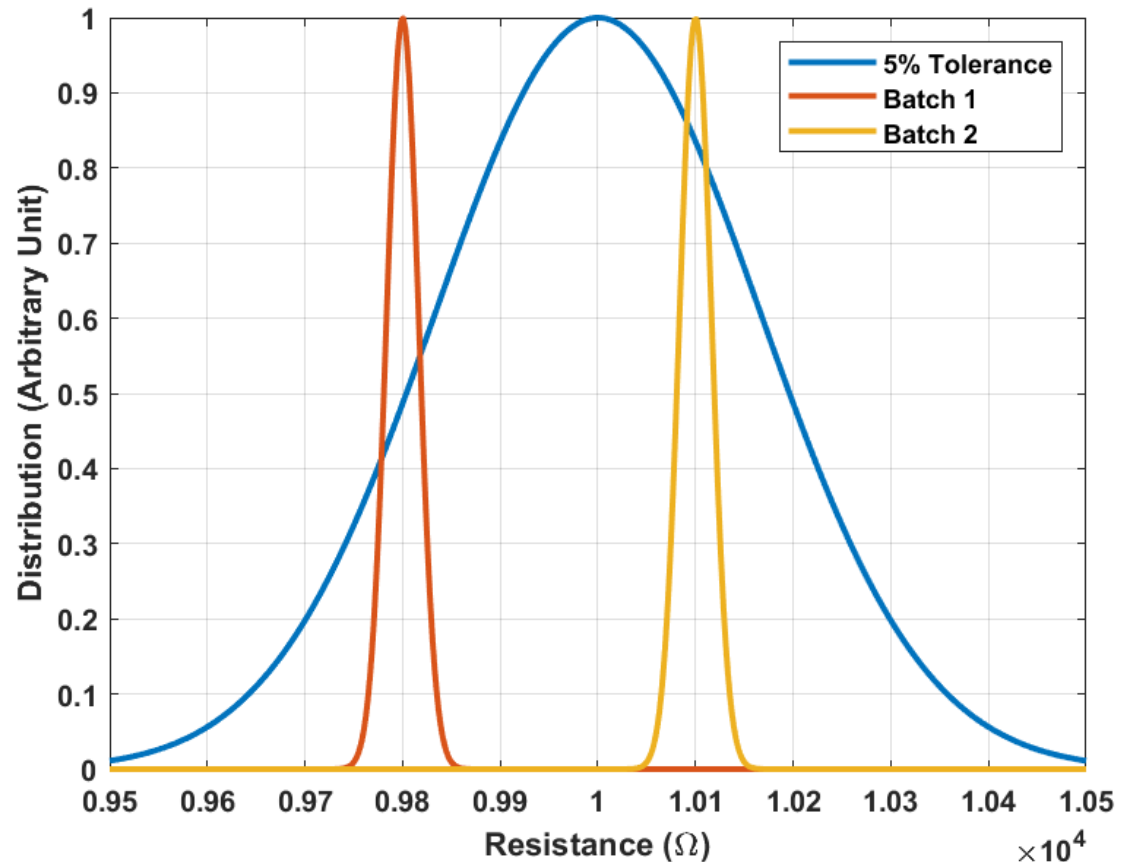If R_f and R_i varies by 5% each, the resulting gain could vary by as much as 10% from desired value!



How to Achieve Accurate Gain?






- Use resistors from **same batch** (they usually match very well)!
- For example, if the desired R_f/R_i ratio is 4, we use 5 identical resistors:
 - R_f uses 4 resistors, and
 - R_i uses 1 resistor.
 - An accurate gain of 4 can be obtained!
- \Rightarrow Principle exploited in IC design

Significance of Closed Loop Negative Feedback

Repeater to restore signal

Slight signal distortion






Repeater to restore signal

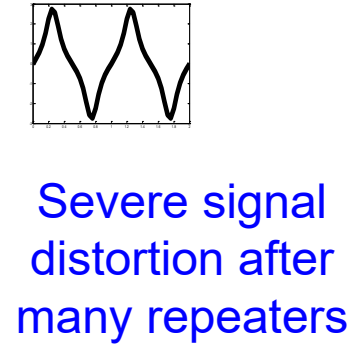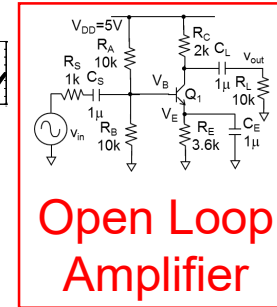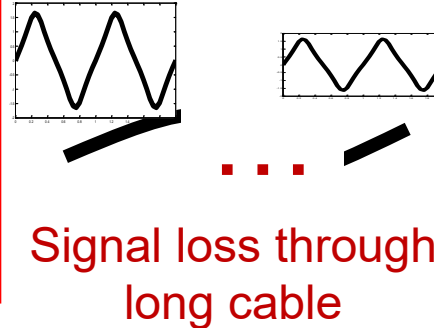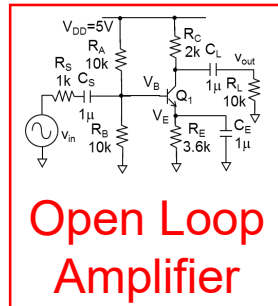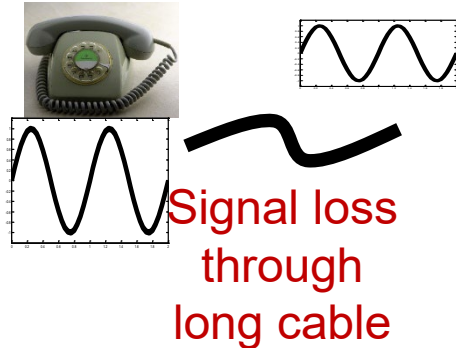

Repeater to restore signal

No distortion

Repeater to restore signal

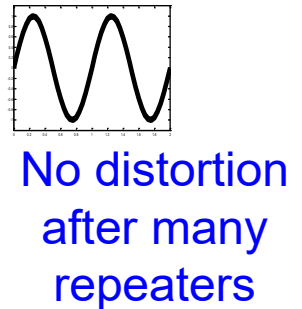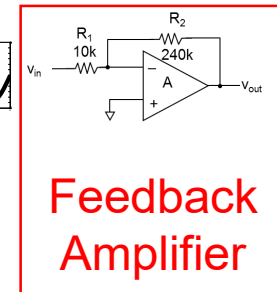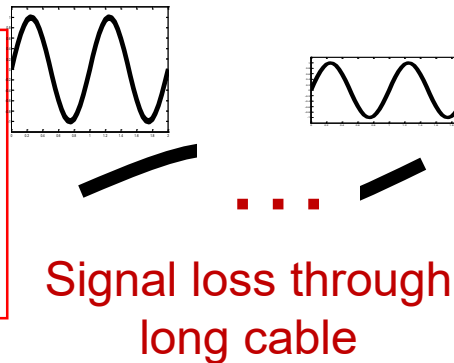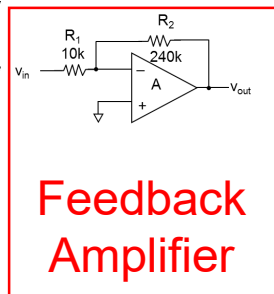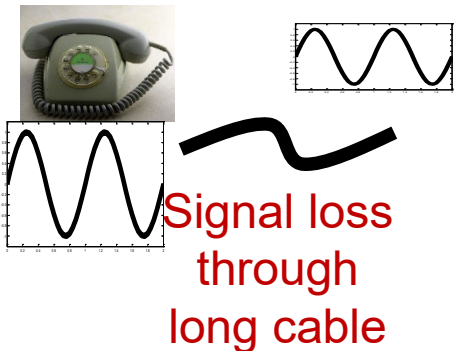

- Harold Stephen Black invented negative feedback amplifier in 1928

Question 1

Given:

- Primary voltage V_P of transformer is 65 V RMS
- Number of turns:
 - Primary windings N_P : 60
 - Secondary windings N_S : 90

Calculate RMS voltage across secondary winding.

$$\frac{V_S}{V_P} = \frac{N_S}{N_P} = \frac{90}{60} = 1.5$$

Therefore, $V_S = 65 \times 1.5 = 97.5 \text{ V RMS}$

Question 2

A given transformer has:

- Primary voltage V_P : 25 V RMS
- Secondary voltage V_S : 90 V RMS
- Secondary windings N_S : 36

Calculate no. of turns in primary winding, N_P .

$$\frac{N_P}{N_S} = \frac{V_P}{V_S} = \frac{25}{90}$$

$$\text{Therefore, } N_P = \frac{25}{90} \times 36 = 10$$

Question 3

A given transformer has:

- Secondary voltage V_S : 100 V RMS
- Primary voltage V_P : 30 V RMS

What is the primary voltage needed to obtain a secondary voltage of 225 V RMS?

$$\frac{V_P}{V_S} = \frac{30}{100} = 0.3$$

Therefore, to obtain $V_S = 225$, we need


$$V_P = 0.3 \times 225 = 67.5 \text{ V RMS}$$

Question 4



A given transformer has:

- Primary voltage $V_P : 325 \angle 0^\circ$
- Secondary side has **series RL load**:
 - $|V_R| = 6 \text{ V}, \quad |V_L| = 8 \text{ V}$

Calculate the turns ratio $\left(\frac{N_P}{N_S}\right)$ of the transformer.

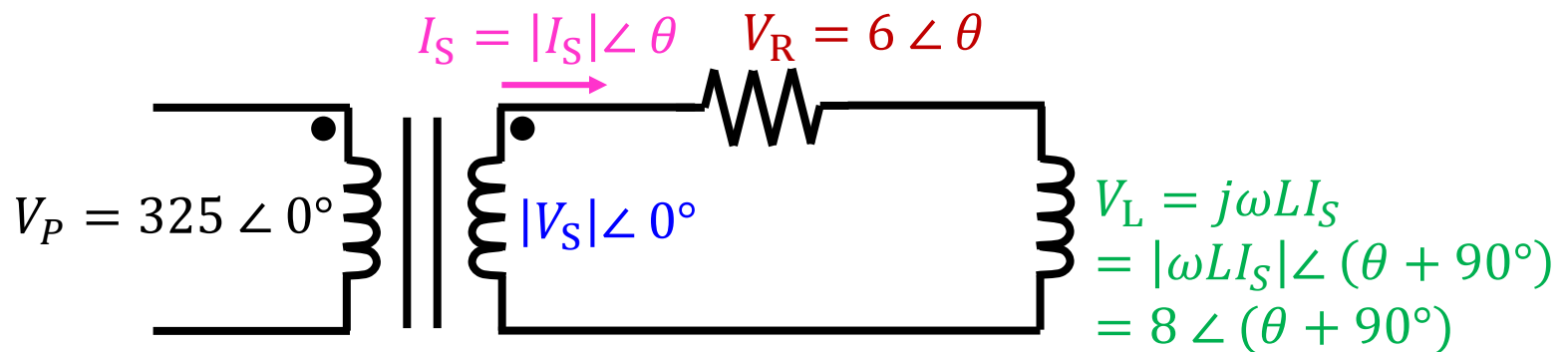

Question 4

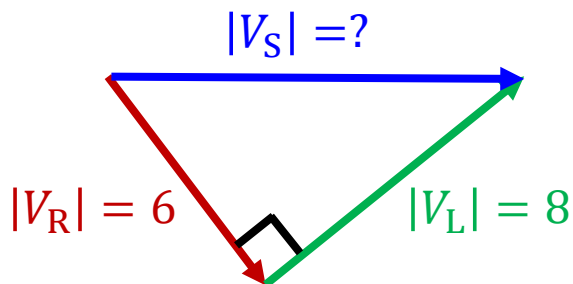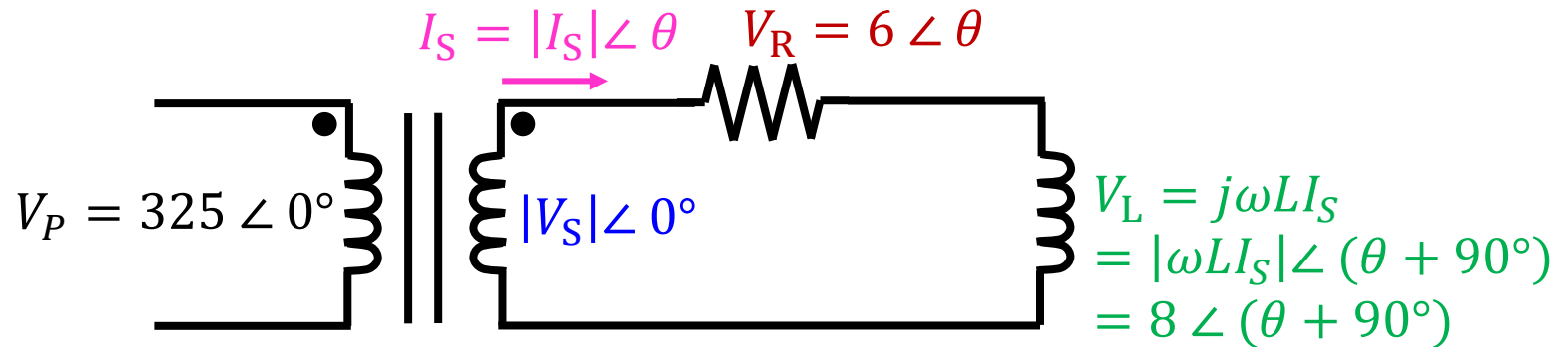


$$|V_S| = \sqrt{6^2 + 8^2} = 10$$

$$\text{Therefore, } \frac{N_P}{N_S} = \frac{|V_P|}{|V_S|} = \frac{325}{10} = 32.5$$


Question 5

Derive an expression for the voltage ripple at load R_L , given that:

- Average load voltage is V_{Load}
- AC power supply's frequency is f_s .

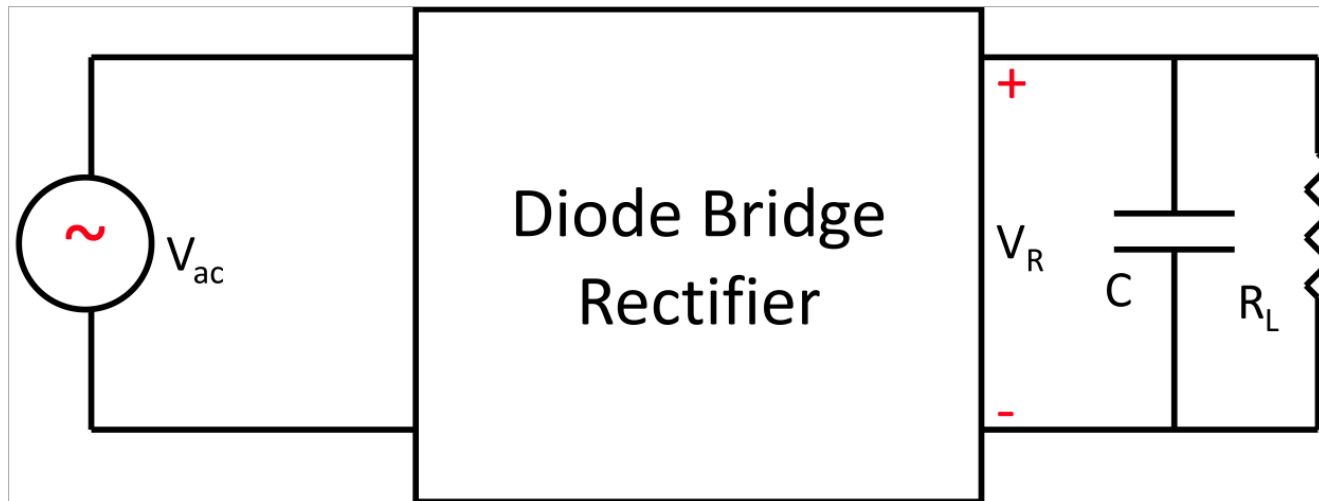

Question 5

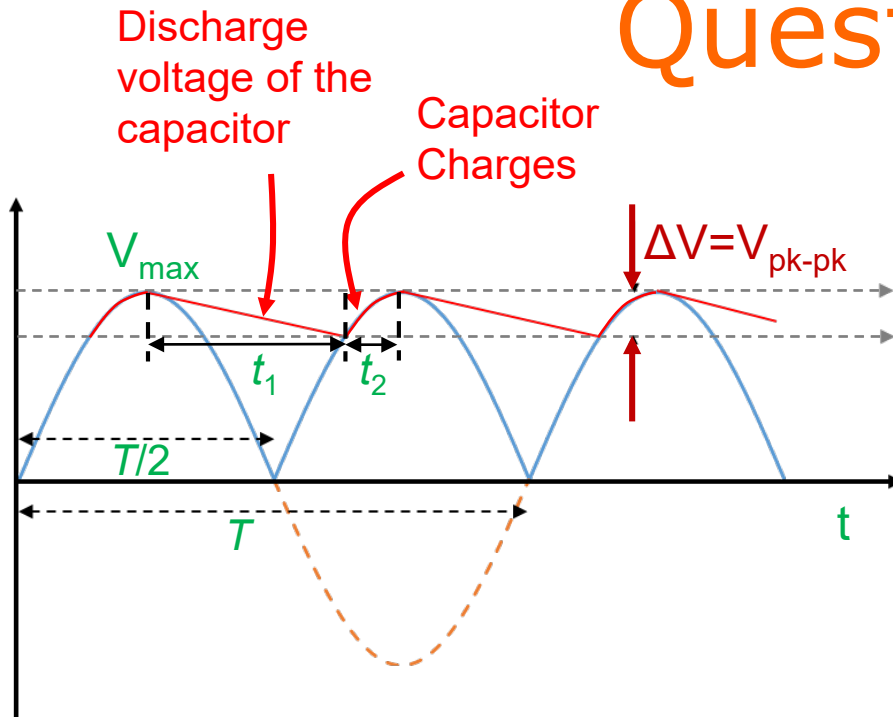

- Let V_{Load} : average load voltage
- Average load current is given by

$$I_L = \frac{V_{Load}}{R_L}$$

- Since it is a full-wave diode bridge rectifier, the pattern repeats **every $T/2$**

- Let ΔV be the peak-to-peak ripple voltage

- $\Delta V = \frac{\Delta Q}{C}$ (from capacitance's definition)

- For small ΔV , $t_1 \approx T/2$. Since $i(t) = \frac{dQ}{dt}$, average current $I_L \approx \frac{\Delta Q}{T/2}$.

- Hence
$$\Delta V \approx \frac{I_L * T/2}{C} = \frac{V_{Load}}{R_L} * \frac{1}{2f_s} * \frac{1}{C}$$

Question 6

Full-wave rectifier with the following:

- Resistive load R_L : $100\ \Omega$
- Average voltage V_{Load} : $9\ \text{V}$
- AC source's frequency f_s : $100\pi\ \text{rad/s}$
- Filter capacitor C : $1.5\ \text{mF}$
- Assume: Ideal diodes with no voltage drop
- Find the voltage ripple

$$\Delta V = \frac{V_{\text{Load}}}{2f_s R_L C} = \frac{9\ \text{V}}{2 \times \frac{100\pi}{2\pi}\ \text{Hz} \times 100\ \Omega \times 1.5\ \text{mF}} = 0.6\ \text{V}$$

Question 7

Full-wave rectifier with the following:

- Average current I_L : 0.2 A
- Average voltage V_{Load} : 15 V
- AC source's frequency f_S : 50 Hz
- Required peak-to-peak ripple $\Delta V \leq 0.5 \text{ V}$
- Assume: Ideal diodes with no voltage drop
- Find the minimum value of the filter capacitor needed

Question 7

- $\Delta V = \frac{V_{Load}}{2f_s R_L C} = \frac{I_L}{2f_s C}$
- $I_L = 0.2 \text{ A}$, $f_s = 50 \text{ Hz}$, and we need $\Delta V \leq 0.5 \text{ V}$

Therefore,

$$0.5 \geq \frac{I_L}{2f_s C}$$

$$C \geq \frac{I_L}{2f_s (0.5)} = \frac{0.2}{2 * 50 * 0.5} = 4 \text{ mF}$$

Question 8

- PMDC motor, 12 V source
- No-load speed = 3800 RPM
- Stall torque = 30 mNm

- If now running at 2500 RPM, find
 - a) I_m
 - b) T_{shaft}
 - c) E_b
 - d) Electrical power consumed
 - e) Shaft power
 - f) Power loss in rotor coil

Question 8

- First, find all **unknown motor parameters**

- 3800 RPM $\rightarrow \omega_{\text{no-load}} = 398 \text{ rad/s}$

- Recall that:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

- At **no-load**, $I_m \approx 0$ since $T_{\text{shaft}} \approx 0$


❖ Hence, $V_m \approx K_e \omega_{\text{no-load}} \rightarrow K_e \approx \frac{12}{398} = 30 \frac{\text{mV}}{\text{rad/s}}$

❖ For PMDC motor, $K_t = K_e = 30 \frac{\text{mNm}}{\text{A}}$

- At **stall condition**, $T_{\text{stall}} = 30 \text{ mNm}$

❖ $I_{\text{stall}} = \frac{T_{\text{stall}}}{K_t} = 1 \text{ A}$

❖ Since $\omega_{\text{stall}} = 0$, $I_{\text{stall}} = \frac{V_m}{R_m} \rightarrow R_m = \frac{12 \text{ V}}{1 \text{ A}} = 12 \Omega$

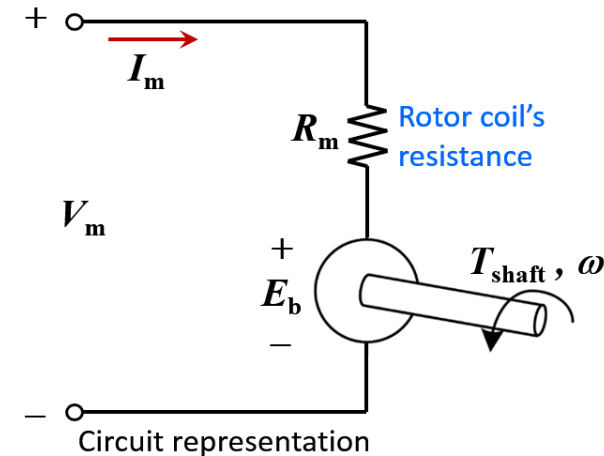

Question 8

At 2500 RPM:

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

a) Find $I_{2500 \text{ RPM}}$ and b) $T_{2500 \text{ RPM}}$

$$\omega_{2500 \text{ RPM}} = 261.8 \text{ rad/s}$$

$$\begin{aligned} \text{a) } I_{2500 \text{ RPM}} &= \frac{V_m}{R_m} - \frac{K_e \omega_{2500 \text{ RPM}}}{R_m} \\ &= \frac{12}{12} - \frac{0.03 \times 261.8}{12} = 0.346 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{b) } T_{2500 \text{ RPM}} &= K_t I_{2500 \text{ RPM}} \\ &= 0.03 \times 0.346 = 10.4 \text{ mNm} \end{aligned}$$

Question 8

c) Find back emf $E_{2500 \text{ RPM}}$

$$E_{2500 \text{ RPM}} = K_e \omega_{2500 \text{ RPM}} = 7.85 \text{ V}$$

d) Find total electrical power consumed P_e

$$P_e = V_m \times I_{2500 \text{ RPM}} = 4.15 \text{ W}$$

Question 8

e) Find shaft power P_{shaft}

$$P_{\text{shaft}} = T_{2500 \text{ RPM}} \times \omega_{2500 \text{ RPM}} = 2.72 \text{ W}$$

f) Find power loss in rotor coil

$$P_{\text{loss}} = R_m \times (I_{2500 \text{ RPM}})^2 = 1.44 \text{ W}$$

Question 9

- Same motor as Q8
- Load condition unchanged
 - (i.e., same torque as $T_{2500 \text{ RPM}}$ previously)
- New desired speed = 1500 RPM
- Find:
 - a) Rotor current I_m and the required V_m
 - b) PWM duty cycle if DC source still 12 V
 - c) T_{on} and T_{off} if PWM frequency = 5 kHz
 - d) Electrical power consumed
 - e) Power loss in rotor coil

Question 9

a) Find current I_m and the required V_m


Same load means **same torque** as $T_{2500 \text{ RPM}}$ previously, hence **current remains unchanged** at

$$I_m = 0.346 \text{ A}$$

$$\omega_{1500 \text{ RPM}} = 157.1 \text{ rad/s}$$

$$E_b = K_e \omega = 4.71 \text{ V}$$

$$V_m = R_m I_m + E_b = 8.86 \text{ V}$$

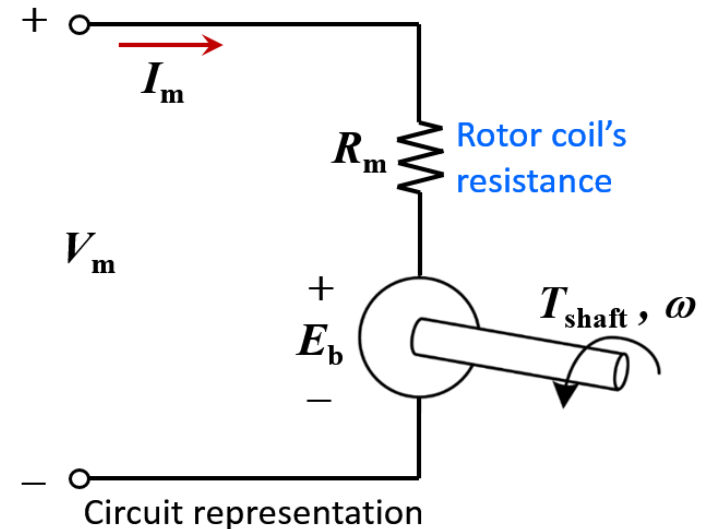

Question 9

b) Find PWM duty cycle if DC source is 12 V

$$\text{Duty Cycle} = \frac{8.86}{12} = 73.8\%$$

c) T_{on} and T_{off} if PWM frequency = 5 kHz

$$T_p = \frac{1}{5000} = 200 \mu\text{s}$$

$$T_{\text{on}} = 0.738 \times 200 \mu\text{s} = 147.6 \mu\text{s}$$

$$T_{\text{off}} = T_p - T_{\text{on}} = 52.4 \mu\text{s}$$

Question 9

d) Find total electrical power consumed

$$P_e = V_m \times I_m = 8.86 \times 0.346 = 3.07 \text{ W}$$

e) Find power loss in rotor coil

$$P_{\text{loss}} = R_m \times (I_m)^2 = 1.44 \text{ W}$$

(same as Q8 because load torque and I_m unchanged!)

Question 10

- PMDC motor with fan
- Fan's load torque $T_L = 0.05\omega + 0.001\omega^2$
- $K_t = 2.42 \text{ Nm/A}$
- $R_m = 0.2 \Omega$
- 50 V DC power supply

- Find:
Speed of fan

Question 10

Recall that:

$$T_{\text{shaft}} = K_t I_m$$

$$I_m = \frac{V_m}{R_m} - \frac{K_e \omega}{R_m}$$

For PMDC motor:

$$K_t = K_e$$

Therefore:

$$T_{\text{shaft}} = 2.42 \times \left(\frac{50}{0.2} - \frac{2.42}{0.2} \omega \right) = 605 - 29.3\omega$$

Question 10

Since $T_{\text{shaft}} = T_L = 0.05\omega + 0.001\omega^2$

$$605 - 29.3\omega = 0.05\omega + 0.001\omega^2$$
$$\omega^2 + 29350\omega - 605000 = 0$$

Solution of quadratic equation:


$$\omega = +20.6 \text{ or } -29371$$

Keeping the positive value, we have

$$\omega = 20.6 \text{ rad/s} \rightarrow 197 \text{ RPM}$$


Question 11

- Calculate all **voltage drops** and **currents** in this circuit, and label the currents' **directions** & voltage **polarities**
- Calculate the overall voltage gain of this amplifier circuit (A_V), both (in **V/V**) and in units of decibels (**dB**)

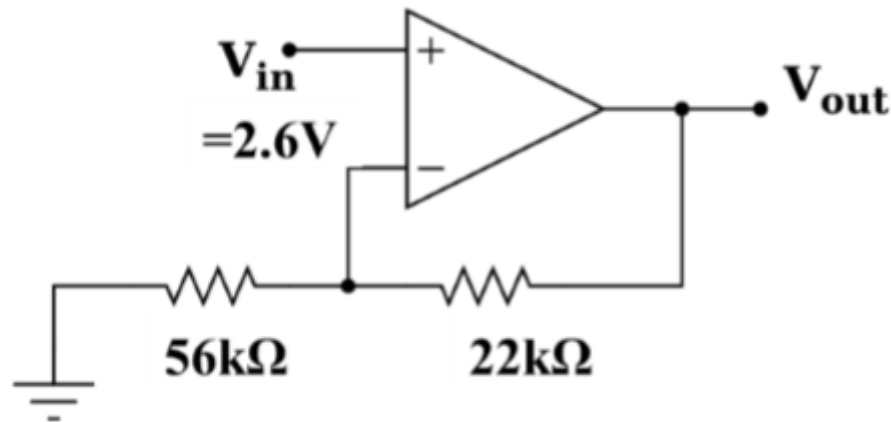

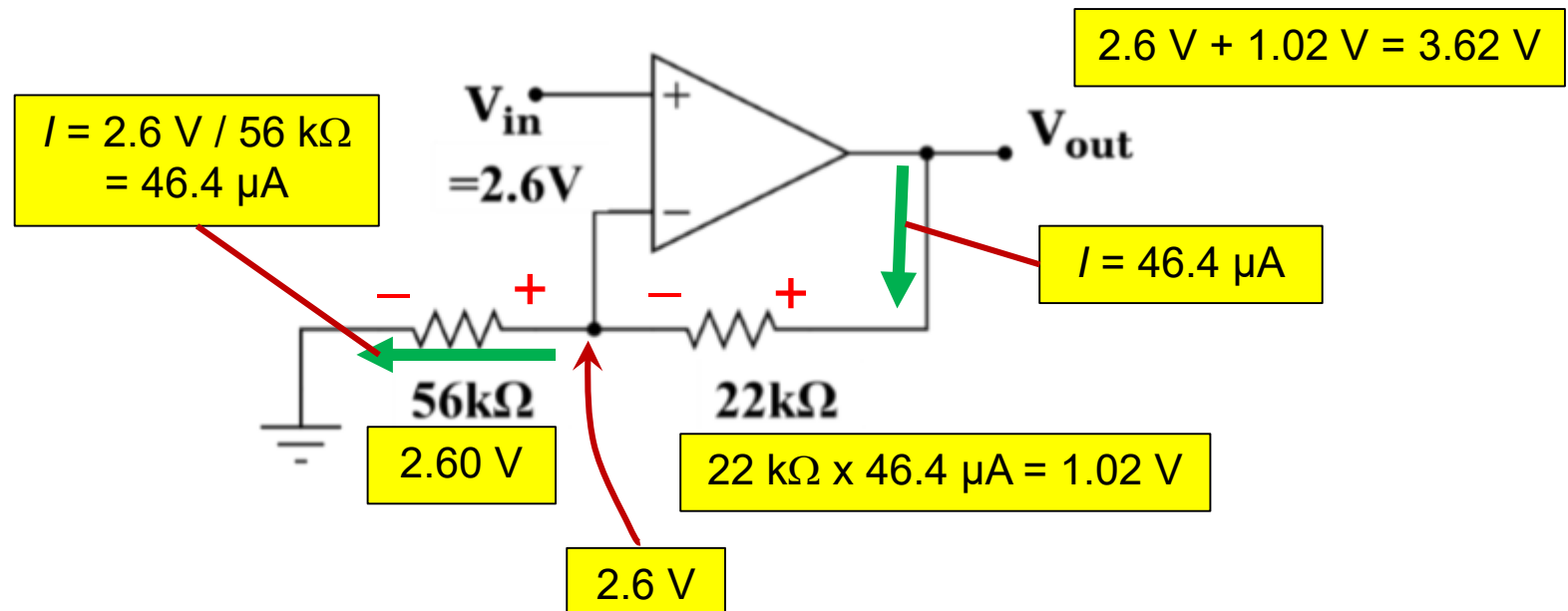Question 11


- Opamp's golden rule: $V_+ \approx V_-$
- No current entering '+' & '-' inputs




- Gain $= \frac{V_{out}}{V_{in}} = \frac{3.62}{2.6} = 1.39\text{ V/V (Volt per Volt)}$
- Gain in dB $= 20 \log_{10}(1.39) = 2.86\text{ dB}$

Question 12

- Calculate all **voltage drops** and **currents** in this circuit, and label the currents' **directions** & voltage **polarities**
- Calculate the **voltage gain** for **each stage** of this amplifier circuit (both as a ratio and in units of decibels), then calculate the **overall voltage gain**

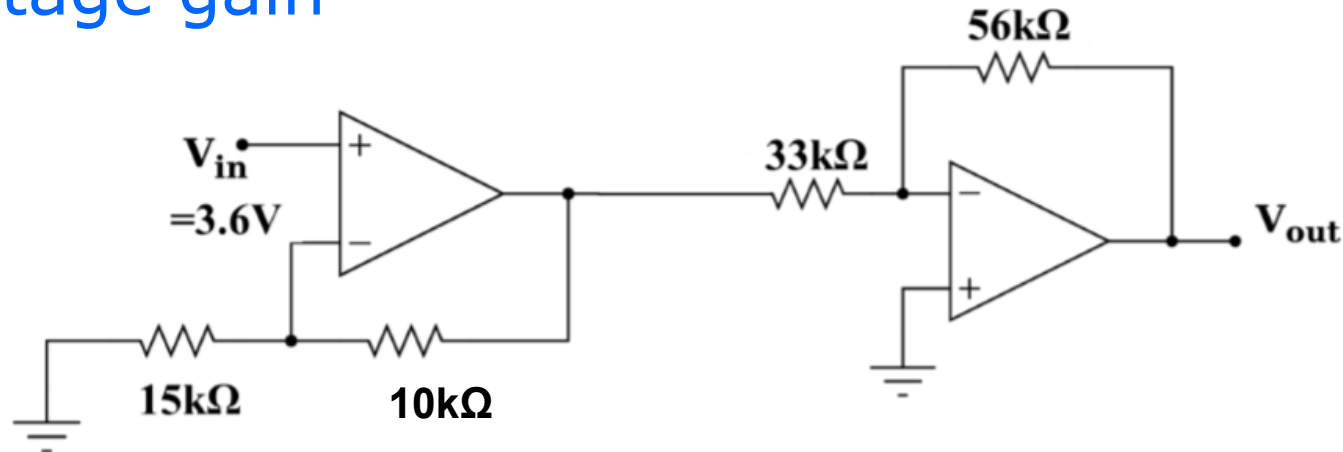


Question 12

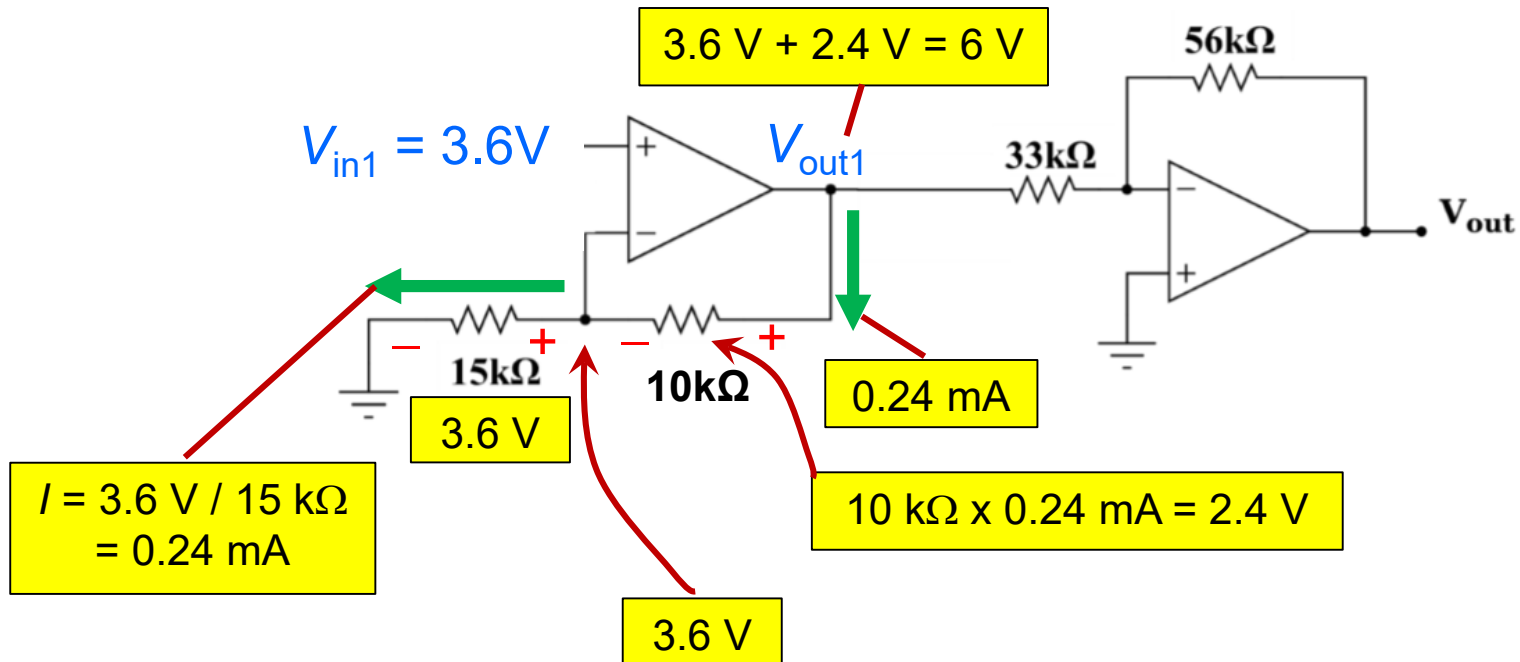

- Gain of 1st stage $= \frac{V_{out1}}{V_{in1}} = \frac{6}{3.6} = 1.67 V/V$
- Gain in dB $= 20 \log_{10} (1.67) = 4.45 dB$


Question 12

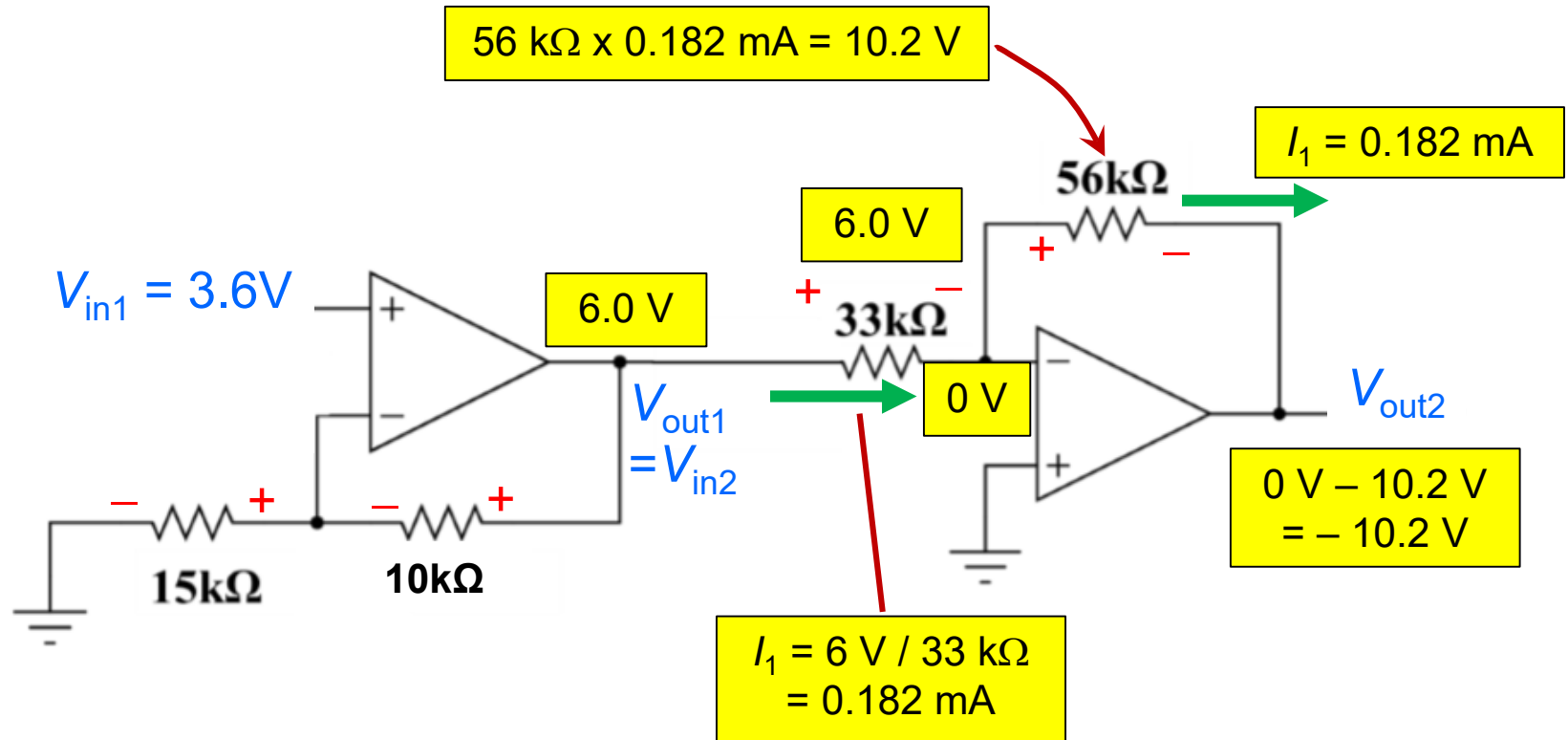

- Gain of 2nd stage = $\frac{V_{out2}}{V_{in2}} = -\frac{10.2}{6} = -1.7 \text{ V/V}$
- Gain in dB = $20 \log_{10} (|-1.7|) = 4.61 \text{ dB}$
- Overall voltage gain = $1.67 \times (-1.7) = -2.84 \text{ V/V} = 9.07 \text{ dB}$

Question 13

- Calculate the voltage gain (V_{out}/V_{in}) of Op Amp 1

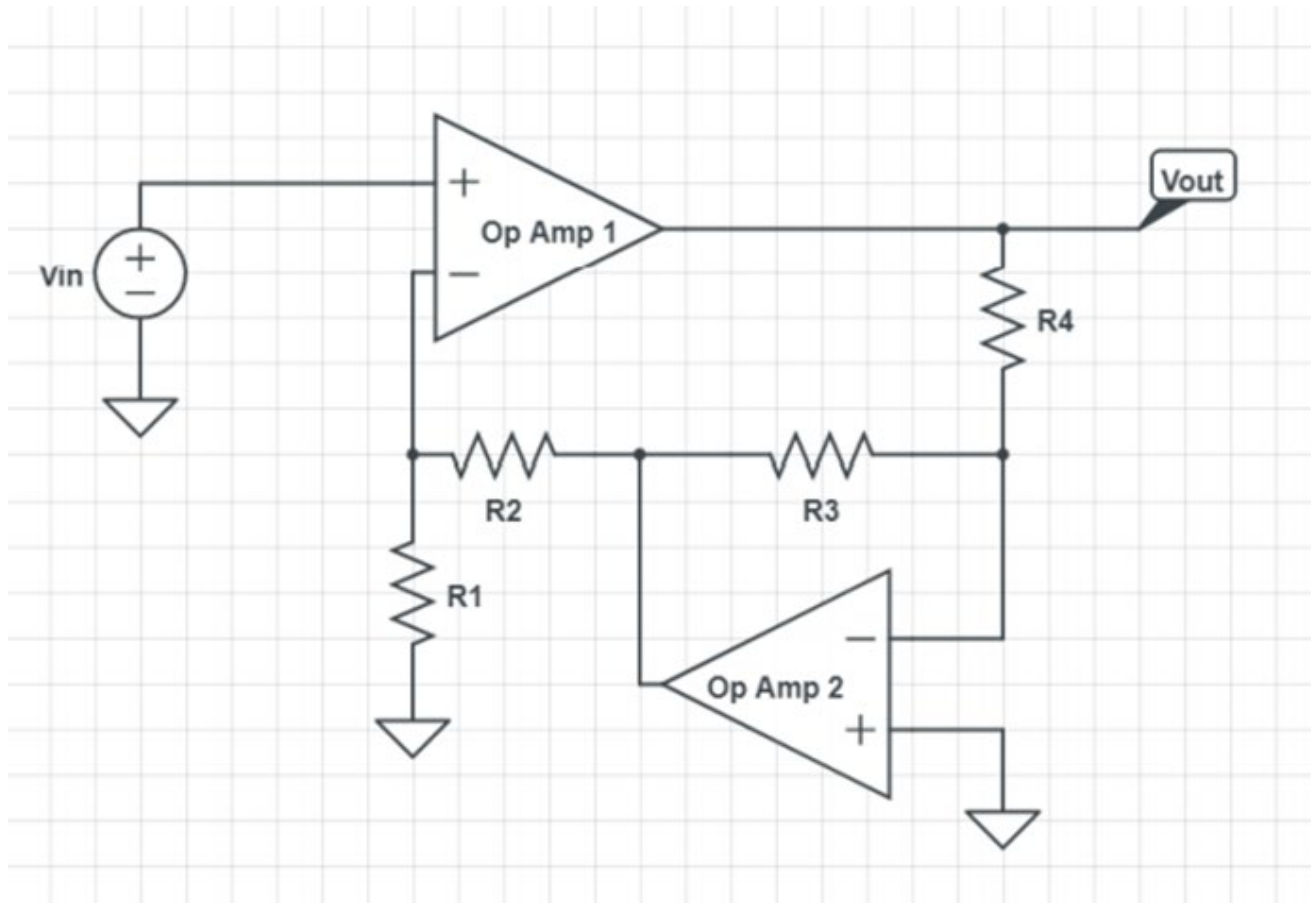


Question 13

- Using op amp Golden rules:

Applying KCL at Node 3,
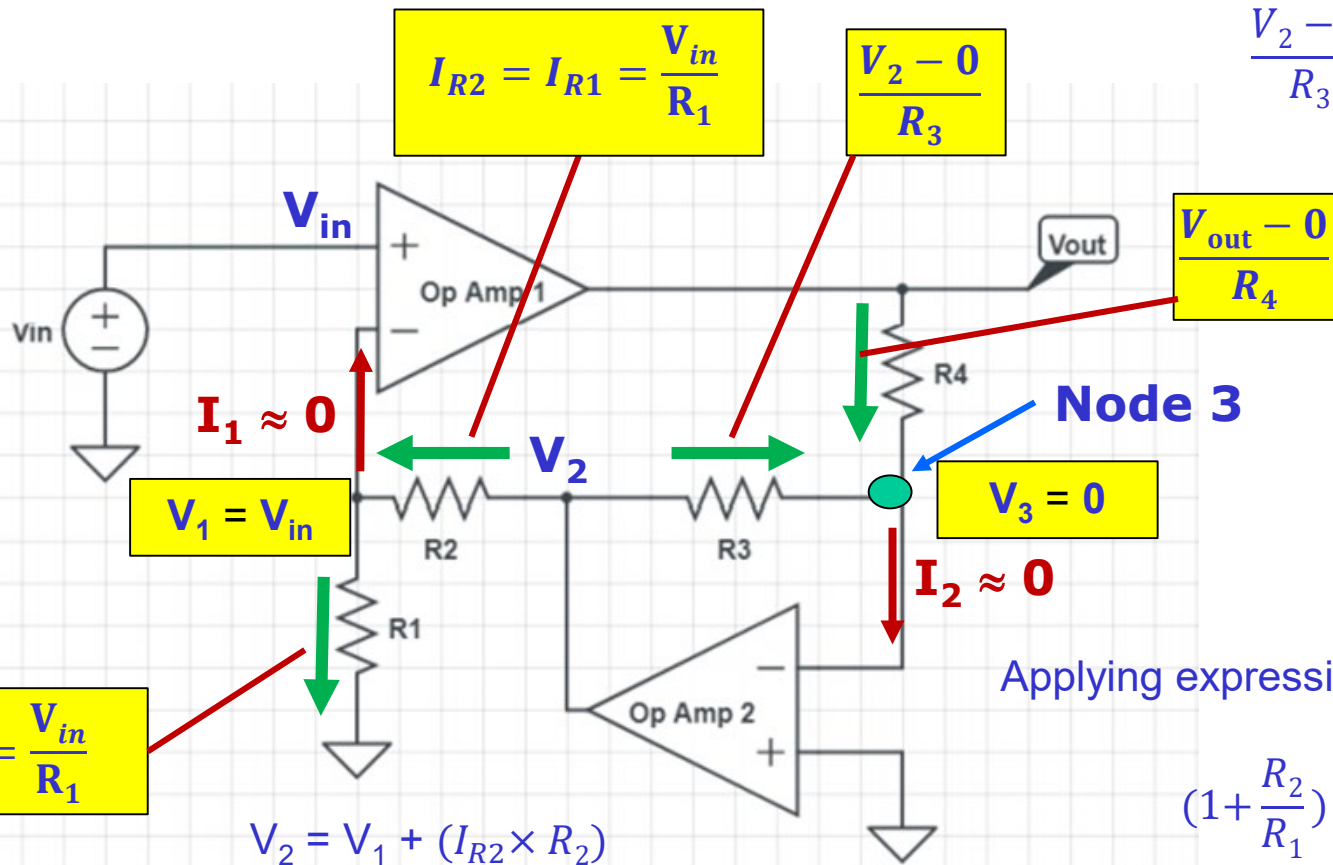
$$\frac{V_2 - 0}{R_3} + \frac{V_{out} - 0}{R_4} = 0$$



Applying expression for V_2 from Eqn 1,


$$\left(1 + \frac{R_2}{R_1}\right) \times \frac{V_{in}}{R_3} = \frac{-V_{out}}{R_4}$$

$$\frac{V_{out}}{V_{in}} = -\left(1 + \frac{R_2}{R_1}\right) \times \frac{R_4}{R_3}$$

$$\begin{aligned} V_2 &= V_1 + (I_{R2} \times R_2) \\ &= V_{in} + \frac{V_{in}}{R_1} \times R_2 = \left(1 + \frac{R_2}{R_1}\right) \times V_{in} \\ &\rightarrow V_2 = \left(1 + \frac{R_2}{R_1}\right) \times V_{in} \text{ ----->Eqn 1} \end{aligned}$$

Question 14

- Derive the expression relating V_{out} and the two inputs, V_1 and V_2
- Design R values such that $V_{out} \propto (V_1 - V_2)$

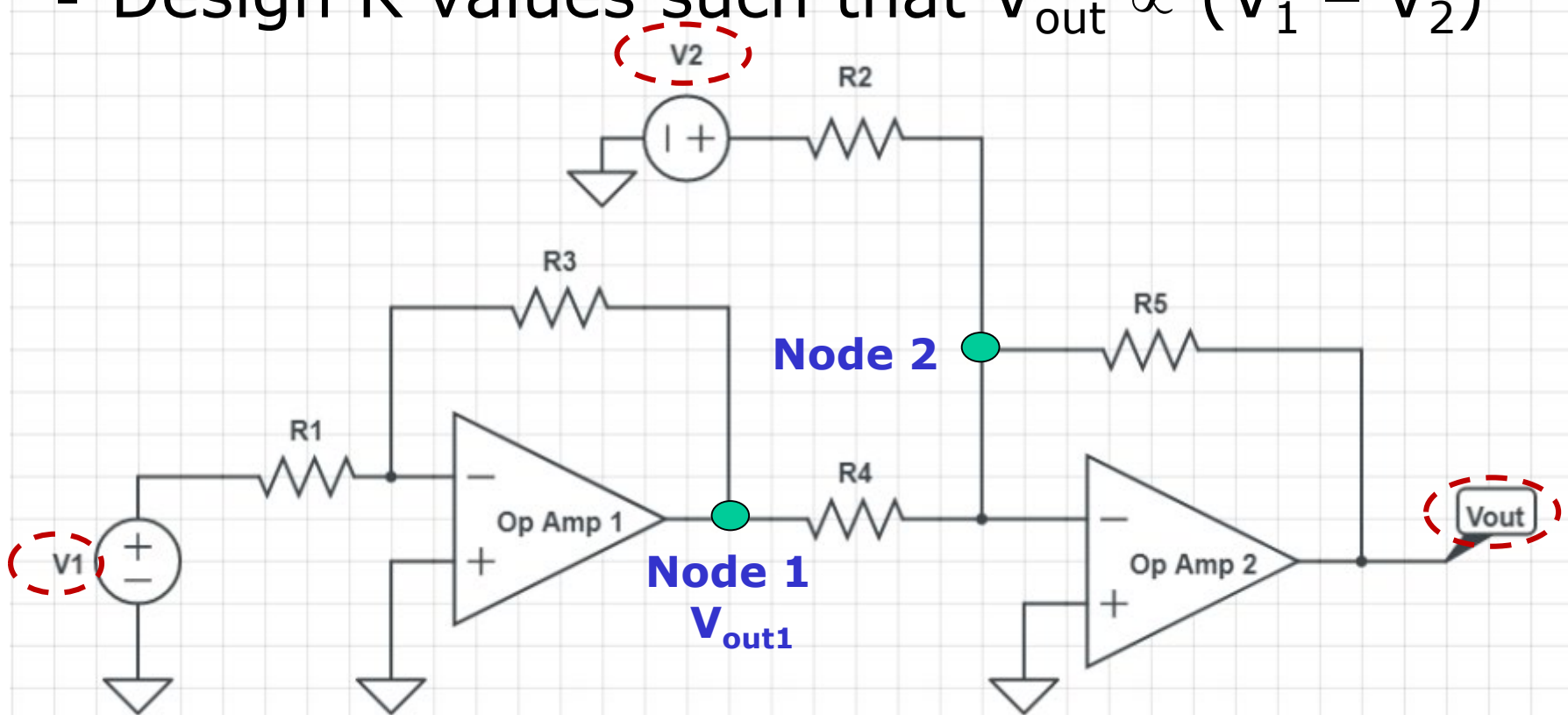

Question 14

If $\frac{R_5 R_3}{R_4 R_1} = \frac{R_5}{R_2}$, which gives $\frac{R_3}{R_4 R_1} = \frac{1}{R_2}$, then

Applying KCL at Node 2,

$$\frac{V_2 - 0}{R_2} + \frac{V_{out1} - 0}{R_4} + \frac{V_{out} - 0}{R_5} = 0$$

$$V_{out} = \left(\frac{R_5}{R_4} * \frac{R_3}{R_1} * V_1 \right) - \left(\frac{R_5}{R_2} * V_2 \right)$$

$$V_{out} = \frac{R_5}{R_2} (V_1 - V_2)$$

$$= K (V_1 - V_2)$$

